



# ALU

Muhammed Adel Ahmed

# Project description

## About The Project:

It is required to design the ALU shown in Fig.1. This ALU can execute arithmetic and logical operations. The operation of the ALU is described by table 1. The output (arithmetic or logical) is selected by the MSB of the selection line, while the required operation is selected by the other 3 bits. It is also required to design flip-flops at the inputs and outputs of the ALU.

 


Fig. 1: ALU Block Diagram

Table 1: ALU Operations

Sel	Operation	Unit
0000	Increment a	Arithmetic
0001	Decrement a	
0010	Multiply a by 2	
0011	Increment b	
0100	Decrement b	
0101	Multiply b by 2	
0110	Add a and b	
0111	Multiply a by 4	
1000	Complement a (1's complement)	Logic
1001	Complement b (1's complement)	
1010	AND	
1011	OR	
1100	XOR	
1101	XNOR	
1110	NAND	
1111	NOR	

## 2. Verilog Code

### ALU Code:

---

#### 1- signed arithmetic and unsigned logic:

```
module alu(  
input [3:0] A,    // 4 – bit input operand A  
input [3:0] B,    // 4 – bit input operand B  
input [3:0] Sel,  // 4 – bit selection signal (Sel[3] determines arithmetic or logical operations)  
output reg [5:0] Y // 6  
– bit output result (result width allows for extended range for arithmetic and logical results)  
);  
  
always @(*) begin  
// Check the most significant bit of Sel (Sel[3])  
// If Sel[3] is 0, perform arithmetic operations  
if (!Sel[3]) begin  
// Use the lower three bits of Sel to choose the arithmetic operation  
case({Sel[2],Sel[1],Sel[0]})  
3'b000 : Y <= $signed(A) + 4'b0001; // Increment A by 1  
3'b001 : Y <= $signed(A) – 4'b0001; // Decrement A by 1  
3'b010 : Y <= $signed(A) << 2;    // Shift A left by 2 (multiply A by 4)  
3'b011 : Y <= $signed(B) + 4'b0001; // Increment B by 1  
3'b100 : Y <= $signed(B) – 4'b0001; // Decrement B by 1  
3'b101 : Y <= $signed(B) << 2;    // Shift B left by 2 (multiply B by 4)  
3'b110 : Y <= $signed(A) + $signed(B); // Add A and B  
3'b111 : Y <= $signed(A) << 4;    // Shift A left by 4 (multiply A by 16)  
endcase  
end  
// If Sel[3] is 1, perform logical operations  
else begin  
// Use the lower three bits of Sel to choose the logical operation  
case({Sel[2],Sel[1],Sel[0]})  
3'b000 : Y <= ~$signed(A);        // Bitwise NOT of A  
3'b001 : Y <= ~$signed(B);        // Bitwise NOT of B  
3'b010 : Y <= $signed(A) & $signed(B); // Bitwise AND of A and B  
3'b011 : Y <= $signed(A) | $signed(B); // Bitwise OR of A and B  
3'b100 : Y <= $signed(A) ^ $signed(B); // Bitwise XOR of A and B  
3'b101 : Y <= ~($signed(A) ^ $signed(B)); // Bitwise XNOR of A and B  
3'b110 : Y <= ~($signed(A) & $signed(B)); // Bitwise NAND of A and B  
3'b111 : Y <= ~($signed(A) + $signed(B)); // Negated sum of A and B (two's complement)  
endcase  
end  
end
```

endmodule

## 2-signed arithmetic and signed logic (Bonus):

```
module alu_2(
    input signed [3:0] A,    // 4-bit input operand A
    input signed [3:0] B,    // 4-bit input operand B
    input signed [3:0] Sel,  // 4-bit selection signal (Sel[3] determines arithmetic or logical operations)
    output reg [5:0] Y // 6-bit output result (result width allows for extended range for arithmetic and logical results)
);
always @(*) begin
    // Check the most significant bit of Sel (Sel[3])
    // If Sel[3] is 0, perform arithmetic operations
    if (!Sel[3]) begin
        // Use the lower three bits of Sel to choose the arithmetic operation
        case({Sel[2], Sel[1], Sel[0]})
            3'b000 : Y <= A + 4'b0001; // Increment A by 1
            3'b001 : Y <= A - 4'b0001; // Decrement A by 1
            3'b010 : Y <= A << 2;    // Shift A left by 2 (multiply A by 4)
            3'b011 : Y <= B + 4'b0001; // Increment B by 1
            3'b100 : Y <= B - 4'b0001; // Decrement B by 1
            3'b101 : Y <= B << 2;    // Shift B left by 2 (multiply B by 4)
            3'b110 : Y <= A + B; // Add A and B
            3'b111 : Y <= A << 4;    // Shift A left by 4 (multiply A by 16)
        endcase
    end
    // If Sel[3] is 1, perform logical operations
    else begin
        // Use the lower three bits of Sel to choose the logical operation
        case({Sel[2], Sel[1], Sel[0]})
            3'b000 : Y <= ~(A);    // Bitwise NOT of A
            3'b001 : Y <= ~(B);    // Bitwise NOT of B
            3'b010 : Y <= (A & B); // Bitwise AND of A and B
            3'b011 : Y <= (A | B); // Bitwise OR of A and B
            3'b100 : Y <= (A ^ B); // Bitwise XOR of A and B
        endcase
    end
end
```

```
3'b101 : Y <= ~(A ^ B); // Bitwise XNOR of A and B
```

```
3'b110 : Y <= ~(A & B); // Bitwise NAND of A and B
```

```
3'b111 : Y <= ~(A + B); // Negated sum of A and B (two's complement)
```

```
endcase
```

```
end
```

```
end
```

```
endmodule
```

## 3. Test Bench Code

### Test Bench Code:

---

```
module alu_tb2;

// Testbench signals
reg [3:0] A;      // 4-bit test input operand A
reg [3:0] B;      // 4-bit test input operand B
reg [3:0] Sel;    // 4-bit test input selection signal
wire [5:0] Y;     // 6-bit test output result (wire)

// Instantiate the ALU module
alu uut (
    .A(A),
    .B(B),
    .Sel(Sel),
    .Y(Y)
);
integer i;
initial begin
    // Display header
    $display("Time\tA\tB\tSel\tY");

    // Initialize inputs
    A = 4'b0000;
    B = 4'b0000;
    Sel = 4'b0000;

    // Apply test cases
    for(i = 1; i <= 30; i = i + 1) begin
        $display("Test Case %d", i);
        A = $random % 16; // Limit to 4-bit values (0-15)
        B = $random % 16; // Limit to 4-bit values (0-15)
        Sel = $random % 16; // Limit to 4-bit values (0-15)
        #10;
        $display("%0t\t%b\t%b\t%b\t", $time, A, B, Sel, Y);
    end

    // Stop simulation
    $stop;
end
endmodule
```

```

module alu_tb;
// Testbench signals
reg [3:0] A;      // 4-bit test input operand A   reg [3:0] B;      // 4-bit test input operand B
reg [3:0] Sel;    // 4-bit test input selection signal   wire [5:0] Y;      // 6-bit test output result (wire)
// Instantiate the ALU module
alu uut ( .A(A),.B(B),.Sel(Sel),.Y(Y)  );
initial begin
    // Display header
    $display("Time\tA\tB\tSel\t\tY (Actual)\tY (Expected)");

    // Apply test vectors for Arithmetic Operations (Sel[3] = 0)
    A = 4'b0010; B = 4'b0001; Sel = 4'b0000;
    #10;
    if(Y == 6'b000011)
        $display("Test Case 1 Passed"); else      $display("Test Case 1 Failed");
    $display("%0t\t%b\t%b\t%b\t\t%b\t\t%b", $time, A, B, Sel, Y, 6'b000011); // A + 1

    A = 4'b0010; B = 4'b0001; Sel = 4'b0001;
    #10;
    if(Y == 6'b000001)
        $display("Test Case 2 Passed"); else  $display("Test Case 2 Failed");
    $display("%0t\t%b\t%b\t%b\t\t%b\t\t%b", $time, A, B, Sel, Y, 6'b000001); // A - 1

    A = 4'b0010; B = 4'b0001; Sel = 4'b0010;
    #10;
    if(Y == 6'b001000)
        $display("Test Case 3 Passed"); else  $display("Test Case 3 Failed");
    $display("%0t\t%b\t%b\t%b\t\t%b\t\t%b", $time, A, B, Sel, Y, 6'b001000); // A << 2

    A = 4'b0010; B = 4'b0001; Sel = 4'b0011; #10;
    if(Y == 6'b000010)
        $display("Test Case 4 Passed"); else  $display("Test Case 4 Failed");
    $display("%0t\t%b\t%b\t%b\t\t%b\t\t%b", $time, A, B, Sel, Y, 6'b000010); // B + 1

    A = 4'b0010; B = 4'b0001; Sel = 4'b0100;#10;
    if(Y == 6'b000000)
        $display("Test Case 5 Passed"); else  $display("Test Case 5 Failed");
    $display("%0t\t%b\t%b\t%b\t\t%b\t\t%b", $time, A, B, Sel, Y, 6'b000000); // B - 1

    A = 4'b0010; B = 4'b0001; Sel = 4'b0101;#10;
    if(Y == 6'b000010)
        $display("Test Case 6 Passed"); else  $display("Test Case 6 Failed");
    $display("%0t\t%b\t%b\t%b\t\t%b\t\t%b", $time, A, B, Sel, Y, 6'b000100); // B << 1

    A = 4'b0010; B = 4'b0011; Sel = 4'b0110; #10;
    if(Y == 6'b000101)
        $display("Test Case 7 Passed"); else  $display("Test Case 7 Failed");
    $display("%0t\t%b\t%b\t%b\t\t%b\t\t%b", $time, A, B, Sel, Y, 6'b000101); // A + B

    A = 4'b0010; B = 4'b0001; Sel = 4'b0111; #10;
    if(Y == 6'b001000)
        $display("Test Case 8 Passed"); else  $display("Test Case 8 Failed");
    $display("%0t\t%b\t%b\t%b\t\t%b\t\t%b", $time, A, B, Sel, Y, 6'b001000); // A << 4

```

```

// Apply test vectors for Logical Operations (Sel[3] = 1)
A = 4'b0010; B = 4'b0001; Sel = 4'b1000; #10;
if(Y == 6'b111101)
    $display("Test Case 9 Passed"); else $display("Test Case 9 Failed");
$display("%0t\t%b\t%b\t%b\t\t%b\t\t%b", $time, A, B, Sel, Y, 6'b111101); // NOT A

A = 4'b0010; B = 4'b0001; Sel = 4'b1001; #10;
if(Y == 6'b111110)
    $display("Test Case 10 Passed"); else $display("Test Case 10 Failed");
$display("%0t\t%b\t%b\t%b\t\t%b\t\t%b", $time, A, B, Sel, Y, 6'b111110); // NOT B

A = 4'b0010; B = 4'b0011; Sel = 4'b1010; #10;
if(Y == 6'b000010)
    $display("Test Case 11 Passed"); else $display("Test Case 11 Failed");
$display("%0t\t%b\t%b\t%b\t\t%b\t\t%b", $time, A, B, Sel, Y, 6'b000010); // A AND B

A = 4'b0010; B = 4'b0011; Sel = 4'b1011;
#10;
if(Y == 6'b000011)
    $display("Test Case 12 Passed");
else
    $display("Test Case 12 Failed");
$display("%0t\t%b\t%b\t%b\t\t%b\t\t%b", $time, A, B, Sel, Y, 6'b000011); // A OR B

A = 4'b0010; B = 4'b0011; Sel = 4'b1100;
#10;
if(Y == 6'b000001)
    $display("Test Case 13 Passed");
else
    $display("Test Case 13 Failed");
$display("%0t\t%b\t%b\t%b\t\t%b\t\t%b", $time, A, B, Sel, Y, 6'b000001); // A XOR B

A = 4'b0010; B = 4'b0011; Sel = 4'b1101;
#10;
if(Y == 6'b111110)
    $display("Test Case 14 Passed");
else
    $display("Test Case 14 Failed");
$display("%0t\t%b\t%b\t%b\t\t%b\t\t%b", $time, A, B, Sel, Y, 6'b111110); // A XNOR B


A = 4'b0010; B = 4'b0011; Sel = 4'b1110;
#10;
if(Y == 6'b111101)
    $display("Test Case 15 Passed");
else
    $display("Test Case 15 Failed");
$display("%0t\t%b\t%b\t%b\t\t%b\t\t%b", $time, A, B, Sel, Y, 6'b111101); // NAND A and B

A = 4'b0010; B = 4'b0011; Sel = 4'b1111;
#10;
if(Y == 6'b111010)
    $display("Test Case 16 Passed");
else
    $display("Test Case 16 Failed");
$display("%0t\t%b\t%b\t%b\t\t%b\t\t%b", $time, A, B, Sel, Y, 6'b111010); // Nor A and B
$stop;
end
endmodule

```




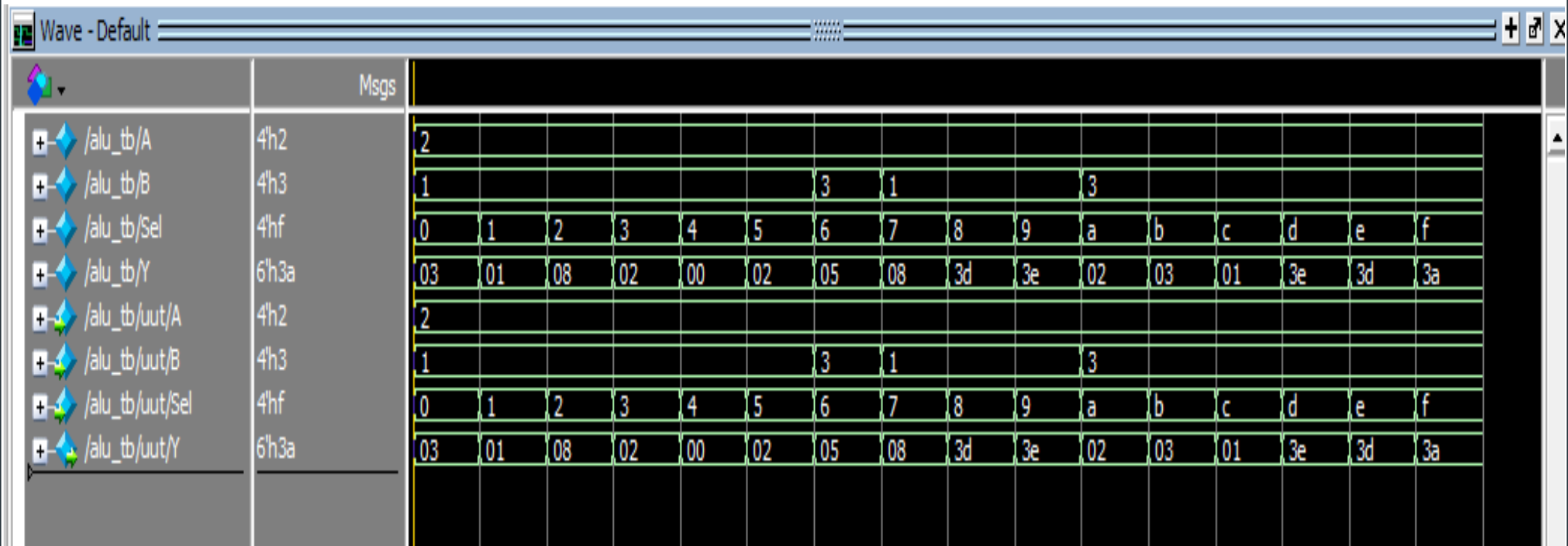
2- different test cases for different inputs:



#	Time	A	B	Sel	Y (Actual)	Y (Expected)
#	Test Case 1	Passed				
#	10	0010	0001	0000	000011	000011
#	Test Case 2	Passed				
#	20	0010	0001	0001	000001	000001
#	Test Case 3	Passed				
#	30	0010	0001	0010	001000	001000
#	Test Case 4	Passed				
#	40	0010	0001	0011	000010	000010
#	Test Case 5	Passed				
#	50	0010	0001	0100	000000	000000
#	Test Case 6	Passed				
#	60	0010	0001	0101	000010	000100
#	Test Case 7	Passed				
#	70	0010	0011	0110	000101	000101
#	Test Case 8	Passed				
#	80	0010	0001	0111	001000	001000
#	Test Case 9	Passed				
#	90	0010	0001	1000	111101	111101
#	Test Case 10	Passed				
#	100	0010	0001	1001	111110	111110
#	Test Case 11	Passed				
#	110	0010	0011	1010	000010	000010
#	Test Case 12	Passed				
#	120	0010	0011	1011	000011	000011
#	Test Case 13	Passed				
#	130	0010	0011	1100	000001	000001
#	Test Case 14	Passed				
#	140	0010	0011	1101	111110	111110
#	Test Case 15	Passed				
#	150	0010	0011	1110	111101	111101
#	Test Case 16	Passed				
#	160	0010	0011	1111	111010	111010

	Msgs	
+ /alu_tb2/A	4'h3	4 3 5 d 6 5 f 8 d 3 0 6 3 2 f a 8 6 c 1 b 5 2 f 9 7 c
+ /alu_tb2/B	4'hd	1 d 2 6 c 5 7 2 5 d a 3 b e 3 c 1 9 6 a 5 a 1 c 8 c 9 1 2
+ /alu_tb2/Sel	4'hd	9 d 1 d 9 a 2 e c 5 0 d 5 d a 2 8 b e b f e 9 f 7 b 0 6 8
+ /alu_tb2/Y	6'h01	3e 01 04 03 04 14 3d 3a 04 05 3a 36 03 28 05 39 3e 39 05 3e 01 3c 3f 0a 08 03
+ /alu_tb2/i	32'h00000002	
+ /alu_tb2/uut/A	4'h3	4 3 5 d 6 5 f 8 d 3 0 6 3 2 f a 8 6 c 1 b 5 2 f 9 7 c
+ /alu_tb2/uut/B	4'hd	1 d 2 6 c 5 7 2 5 d a 3 b e 3 c 1 9 6 a 5 a 1 c 8 c 9 1 2
+ /alu_tb2/uut/Sel	4'hd	9 d 1 d 9 a 2 e c 5 0 d 5 d a 2 8 b e b f e 9 f 7 b 0 6 8
+ /alu_tb2/uut/Y	6'h01	3e 01 04 03 04 14 3d 3a 04 05 3a 36 03 28 05 39 3e 39 05 3e 01 3c 3f 0a 08 03

#	Time	A	B	Sel	Y	#	Test Case	19
#	Test Case			1		#	190	1000 1001 1011 57
#	10	0100	0001	1001	62	#	Test Case	20
#	Test Case			2		#	200	0110 0110 1110 57
#	20	0011	1101	1101	1	#	Test Case	21
#	Test Case			3		#	210	1100 1010 1011 62
#	30	0101	0010	0001	4	#	Test Case	22
#	Test Case			4		#	220	0001 0101 1111 57
#	40	1101	0110	1101	4	#	Test Case	23
#	Test Case			5		#	230	1011 1010 1110 5
#	50	1101	1100	1001	3	#	Test Case	24
#	Test Case			6		#	240	0101 0001 1001 62
#	60	0110	0101	1010	4	#	Test Case	25
#	Test Case			7		#	250	0010 1100 1111 1
#	70	0101	0111	0010	20	#	Test Case	26
#	Test Case			8		#	260	1111 1000 0111 60
#	80	1111	0010	1110	61	#	Test Case	27
#	Test Case			9		#	270	1111 1100 1011 63
#	90	1000	0101	1100	61	#	Test Case	28
#	Test Case			10		#	280	1001 1001 0000 10
#	100	1101	1101	0101	58	#	Test Case	29
#	Test Case			11		#	290	0111 0001 0110 8
#	110	0011	1010	0000	4	#	Test Case	30
#	Test Case			12		#	300	1100 0010 1000 3
#	120	0000	1010	1101	5			
#	Test Case			13				
#	130	0110	0011	1101	58			
#	Test Case			14				
#	140	0011	1011	0101	54			
#	Test Case			15				
#	150	0010	1110	1101	3			
#	Test Case			16				
#	160	1111	0011	1010	3			
#	Test Case			17				
#	170	1010	1100	0010	40			
#	Test Case			18				
#	180	1010	0001	1000	5			
#	Test Case			19				
#	190	1000	1001	1011	57			
-	-	-	-	-	-			

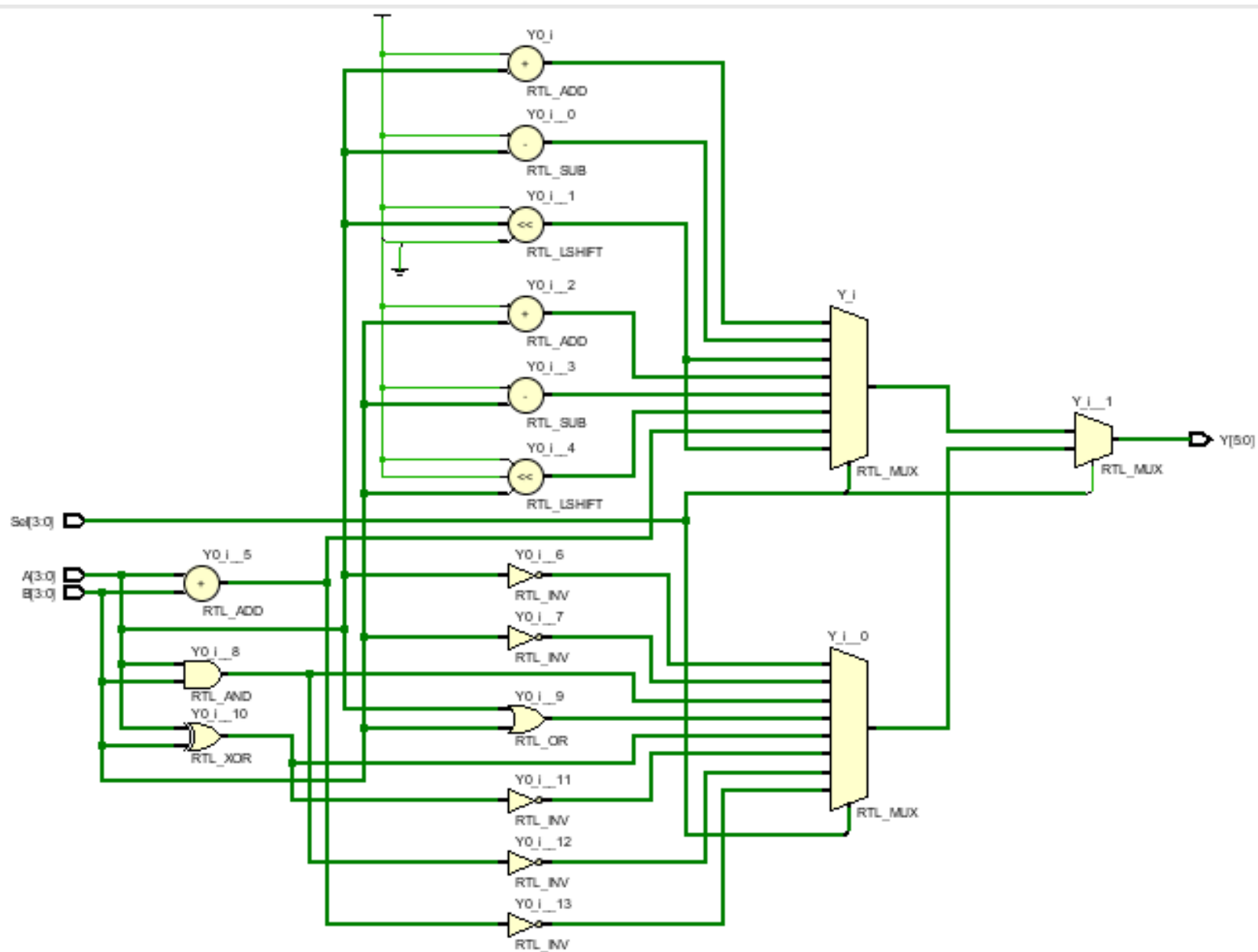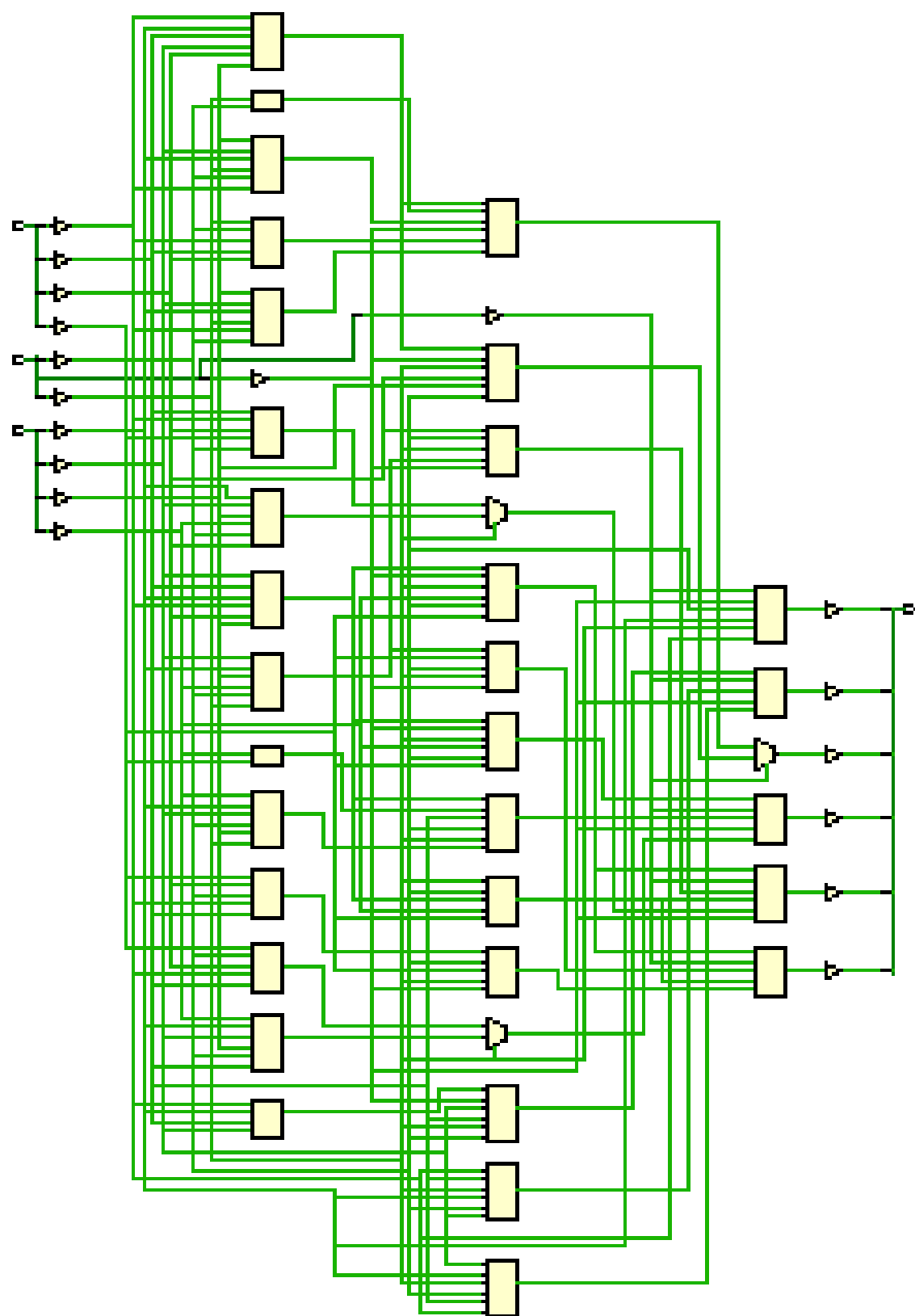


Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:	3.921 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	70.2°C
Thermal Margin:	14.8°C (1.2 W)
Effective θJA:	11.5°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 


				Hierarchy				
Name					1	Slice LUTs (53200)	F7 Muxes (26600)	Bonded IOB (200)
N alu						30	3	18

## 4. Cadence schematics


- In this section, we undertake the individual design of the ALU's schematics for each component and strive to optimize them.
- Our initial step involves designing the essential gates, serving as the primary level of abstraction.
- We will provide a scheme and a symbol for each component used in the design
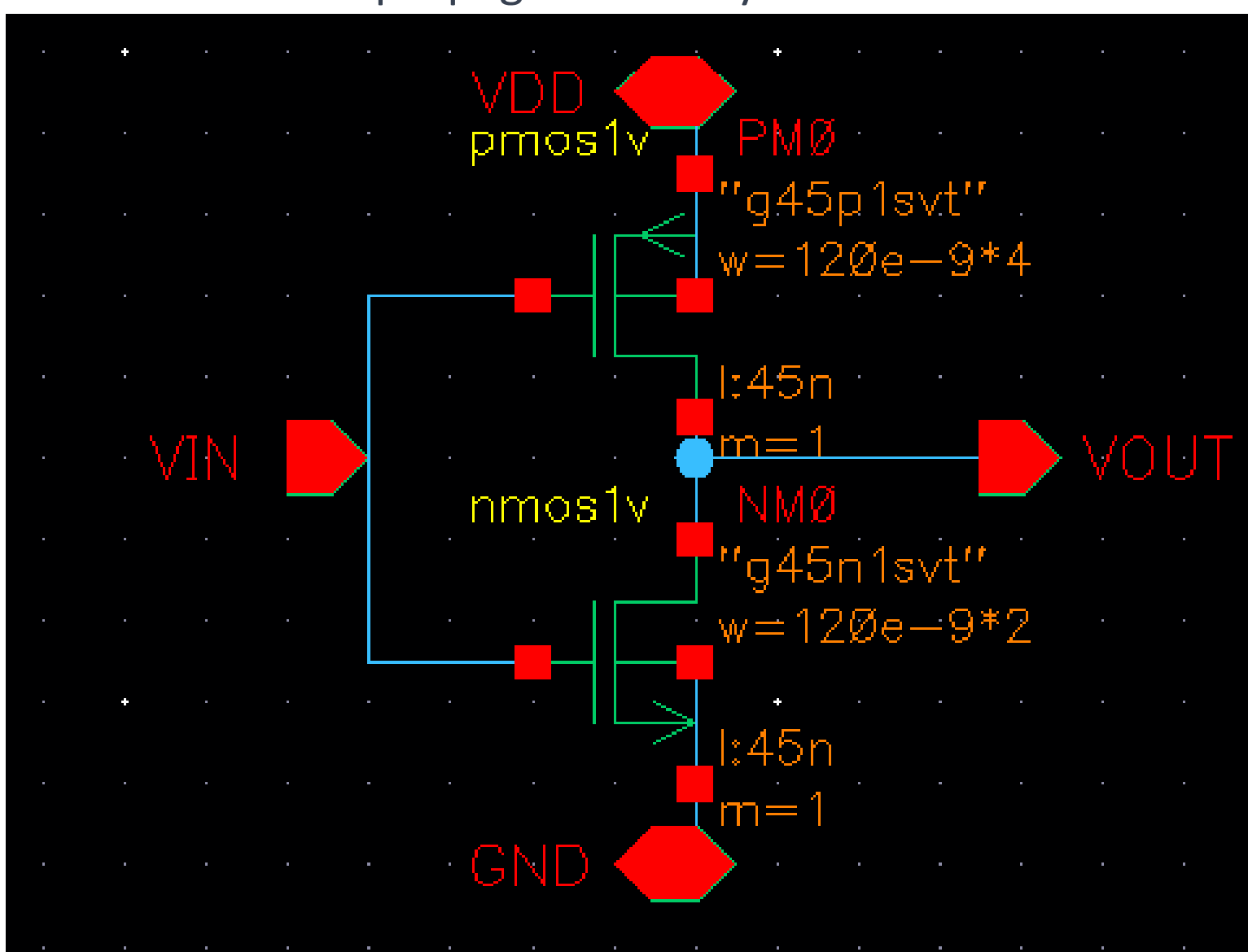
### 4.1 Inverter Schematic

Defining the  $W_p$  and  $W_n$  values is a crucial aspect of the reference inverter, and it is advantageous to assume  $W_p : W_n = (2:1)$ . According to Cadence guidelines, the minimum width available in this technology corresponds to a width of 120nm, considering the minimum length. Therefore, we will assign  $W_n$  as 120nm and set  $W_p$  as 2 times  $W_n$ . Defining  $FP$  (number of fingers for pmos),  $FN$  (number of fingers for nmos), to switch the best value of them to choose the minimum propagation delay.




# 4.1 Inverter Symbol

 

# 4.1 Inverter Testbench

Initially defining the Fp and Fn values:

CDF Parameter	Value	Display
FN	<input type="text" value="1"/>	off <input type="button" value="v"/>
FP	<input type="text" value="2"/>	off <input type="button" value="v"/>
H	<input type="text" value="1"/>	off <input type="button" value="v"/>

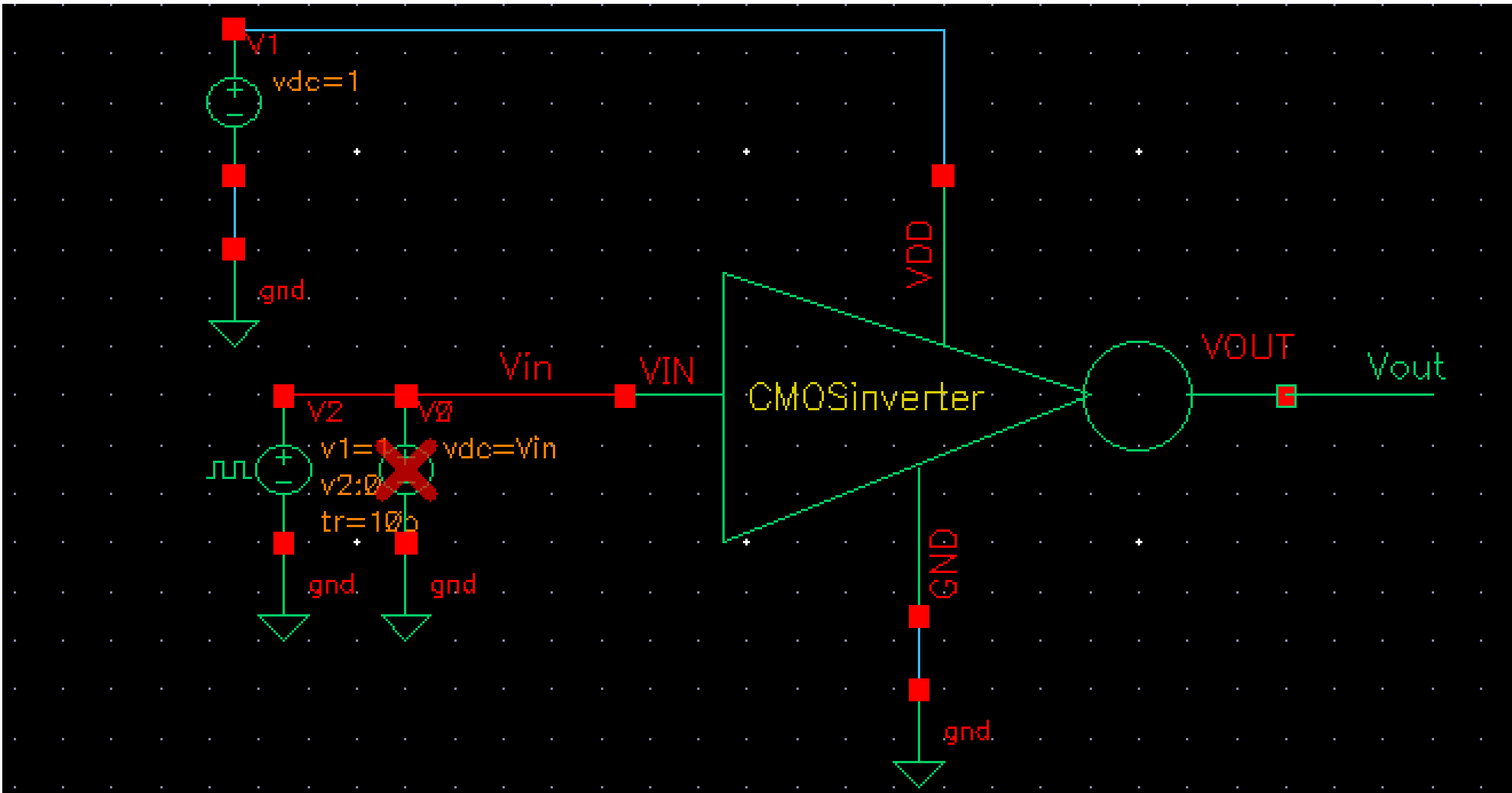


$T_{pd} = 5.80\text{ ps}$

Analyses

Type	Enable	Arguments
1 tran	<input checked="" type="checkbox"/>	0 3n moderate

Outputs

Name/Signal/Expr	Value	Plot	Save	Save Option
1 Vin		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
2 Vout		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
3 tpdf	6.365p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
4 tpdr	5.24293p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
5 tpd	5.80396p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	

 

Try to increase the widths by increase the number of fingers of each:

CDF Parameter		Value	Display
FN		2	off
FP		4	off
H		1	off

So:


$T_{pd} = 5.53\text{ ps}$

Outputs

Name/Signal/Expr	Value	Plot	Save	Save Option
1 Vin		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
2 Vout		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
3 tpdf	5.96527p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
4 tpdr	5.10663p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
5 tpd	5.53595p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
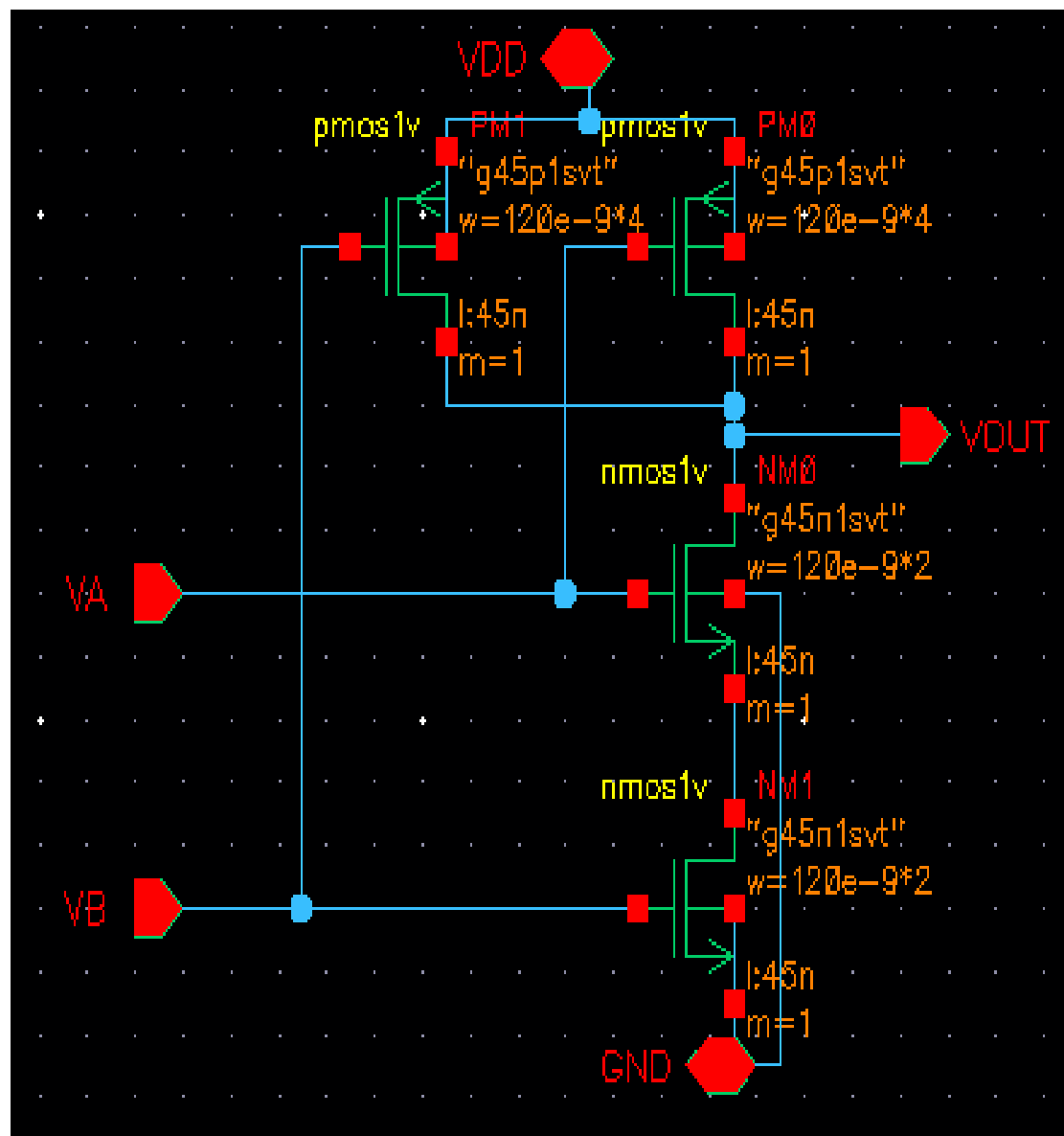
## 4.2 NAND Schematic

- Initially, we determine the gate size based on the reference inverter, considering the worst-case scenario.  $W_n = 2W_{nref} = 320nm$   $W_p = W_{pref} = 320nm$




Library Name	gpd045	off
Cell Name	pmos1v	value
View Name	symbol	off
Instance Name	PM0	off

Add Delete Modify


CDF Parameter	Value	Display
Model Name	g45p1svt	off
Multiplier	pPar("H")	off
Length	45n M	off
Finger Width	120n M	off
Total Width	iPar("fw") * iPar("fingers") M	off
Fingers	pPar("FP")	off
Folding Threshold	10u M	off

## 4.2 NAND Symbol

 



# NAND Testbench

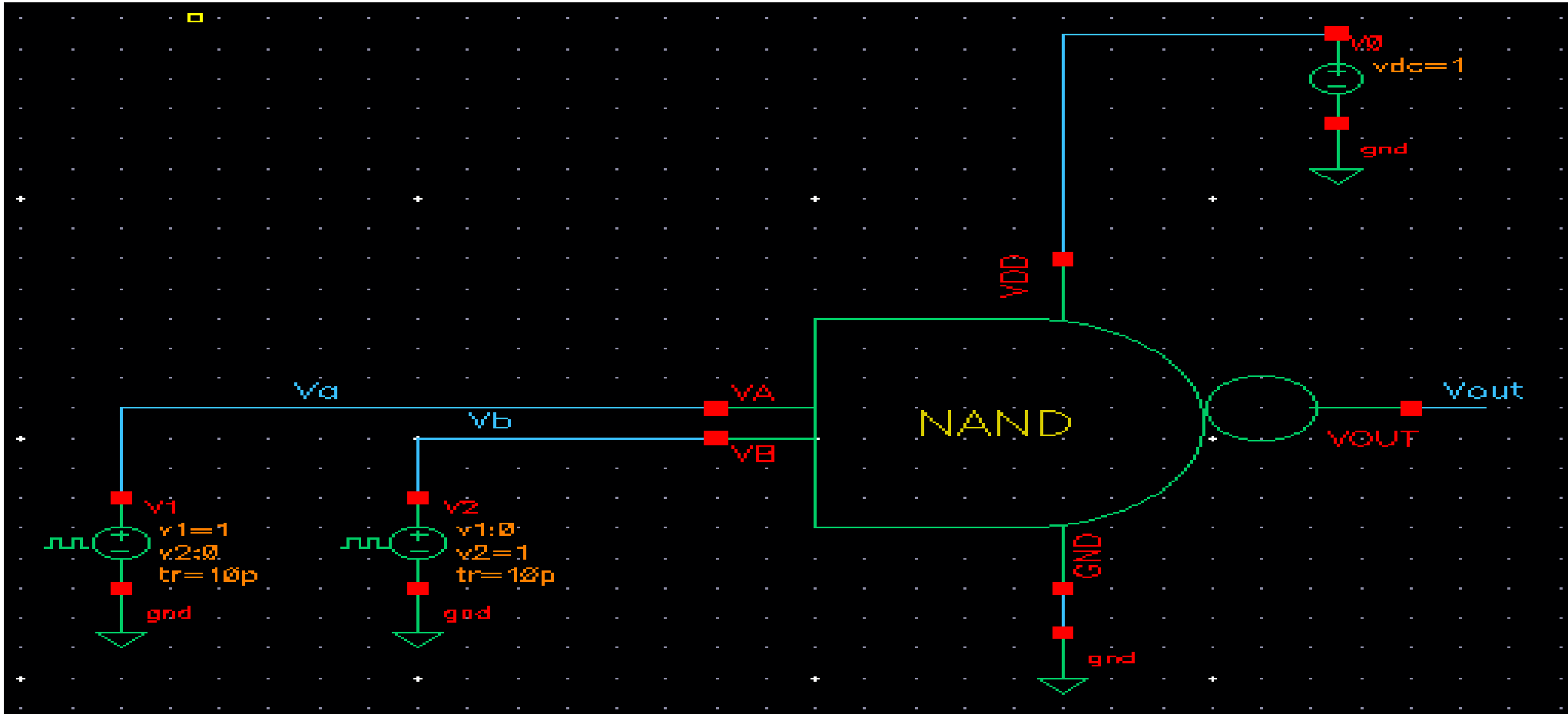

Initially

CDF Parameter		Value
FP		2
FN		1
H		1




So:  $T_{pd} = 9.683\text{ ps}$

CDF Parameter		Value
FP		4
FN		2


So:  $T_{pd} = 9.17\text{ ps}$
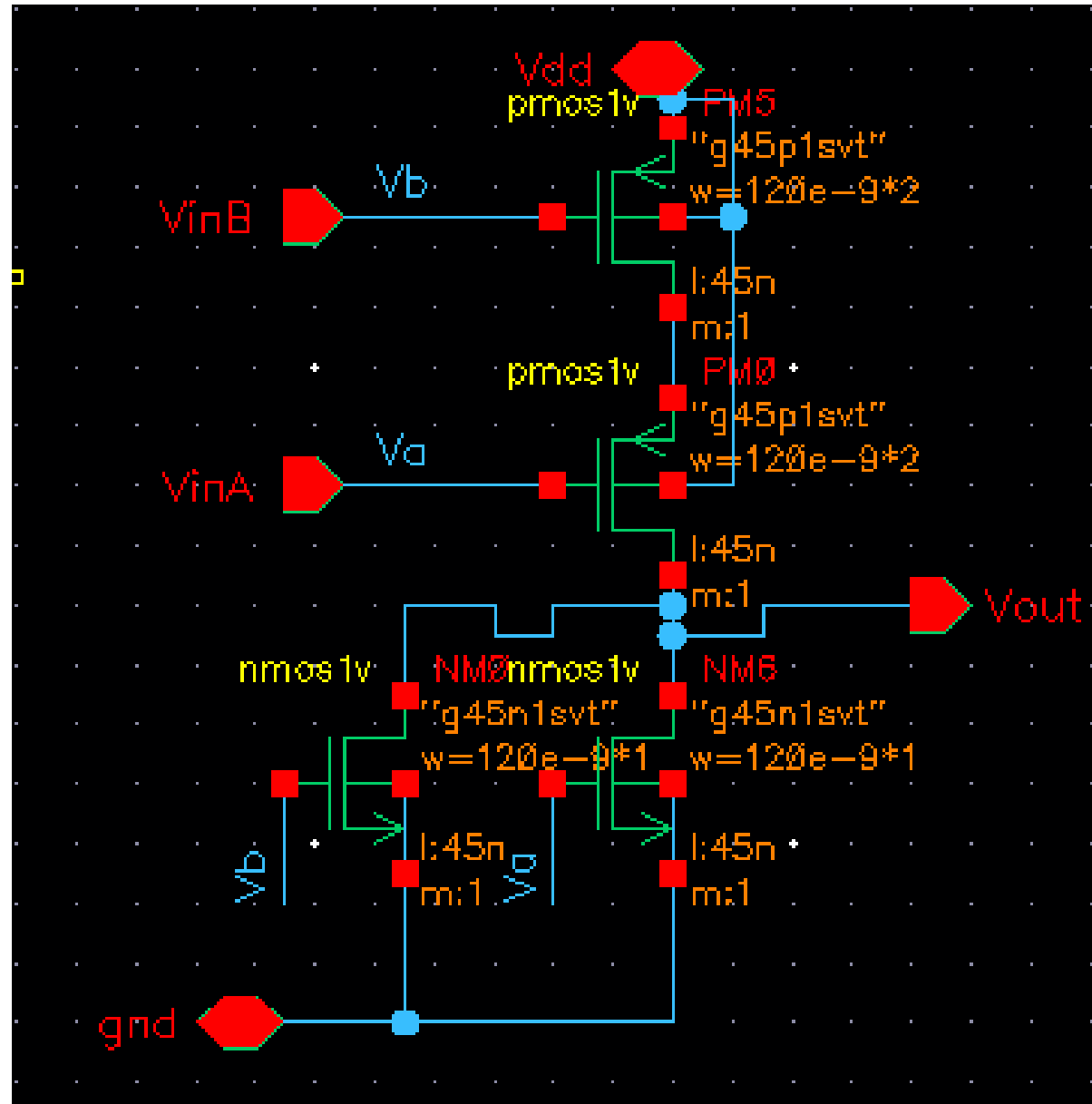
## 4.3 NOR Schematic

- Initially, we determine the gate size based on the reference inverter while taking the worst-case scenario into account.



## 4.3 NOR Symbol

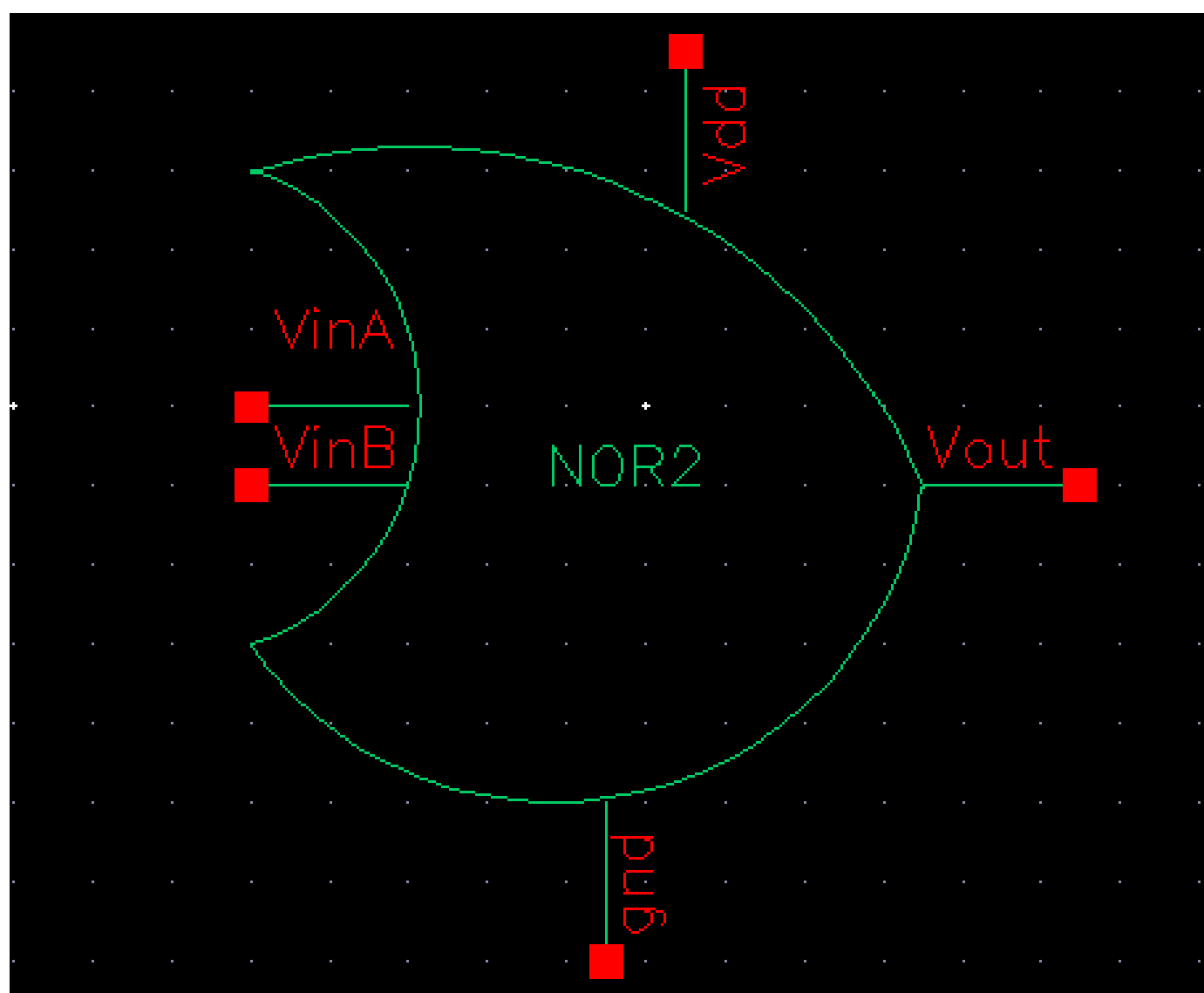

# 4.1 NOR Testbench

CDF Parameter	Value
FN	1
FP	2




So:  $T_{pd} = 12\text{ ps}$

CDF Parameter	Value	Display
FN	2	off
FP	4	off




So:  $T_{pd} = 9.91\text{ ps}$

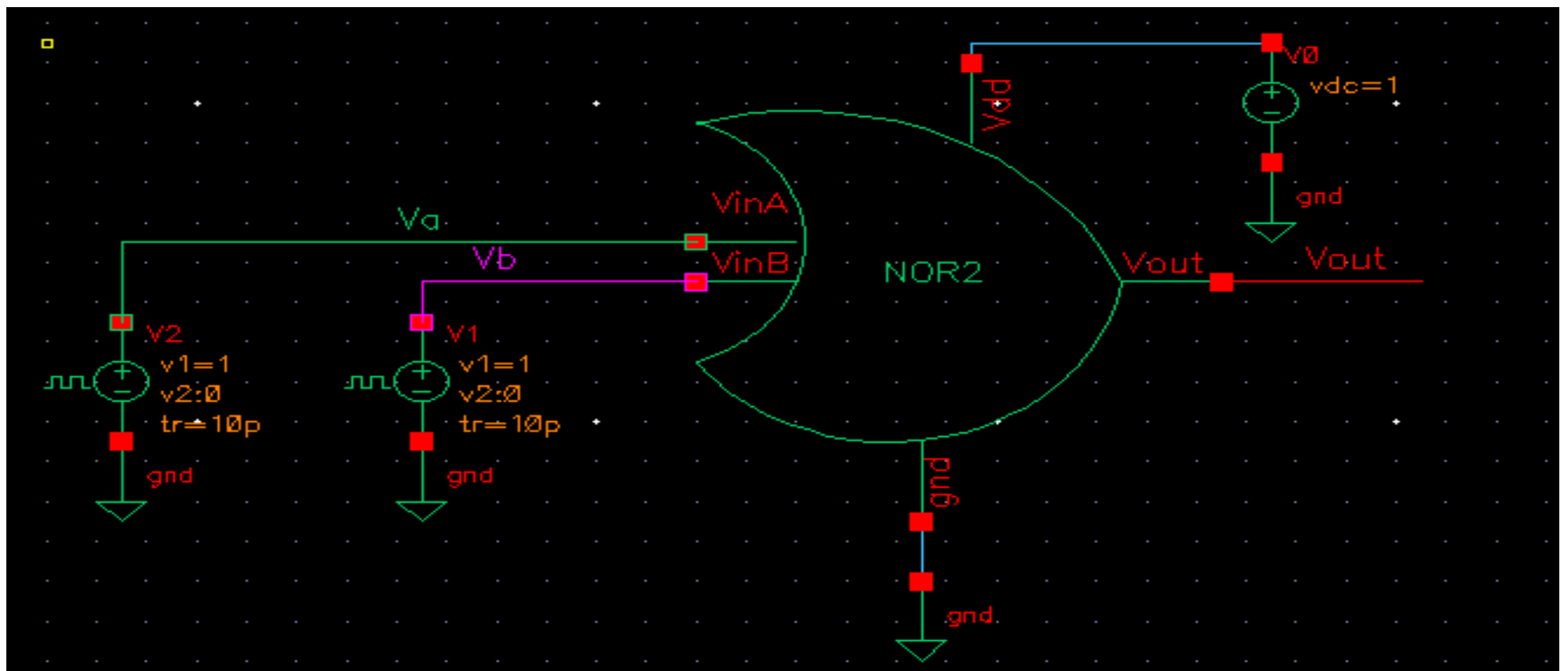

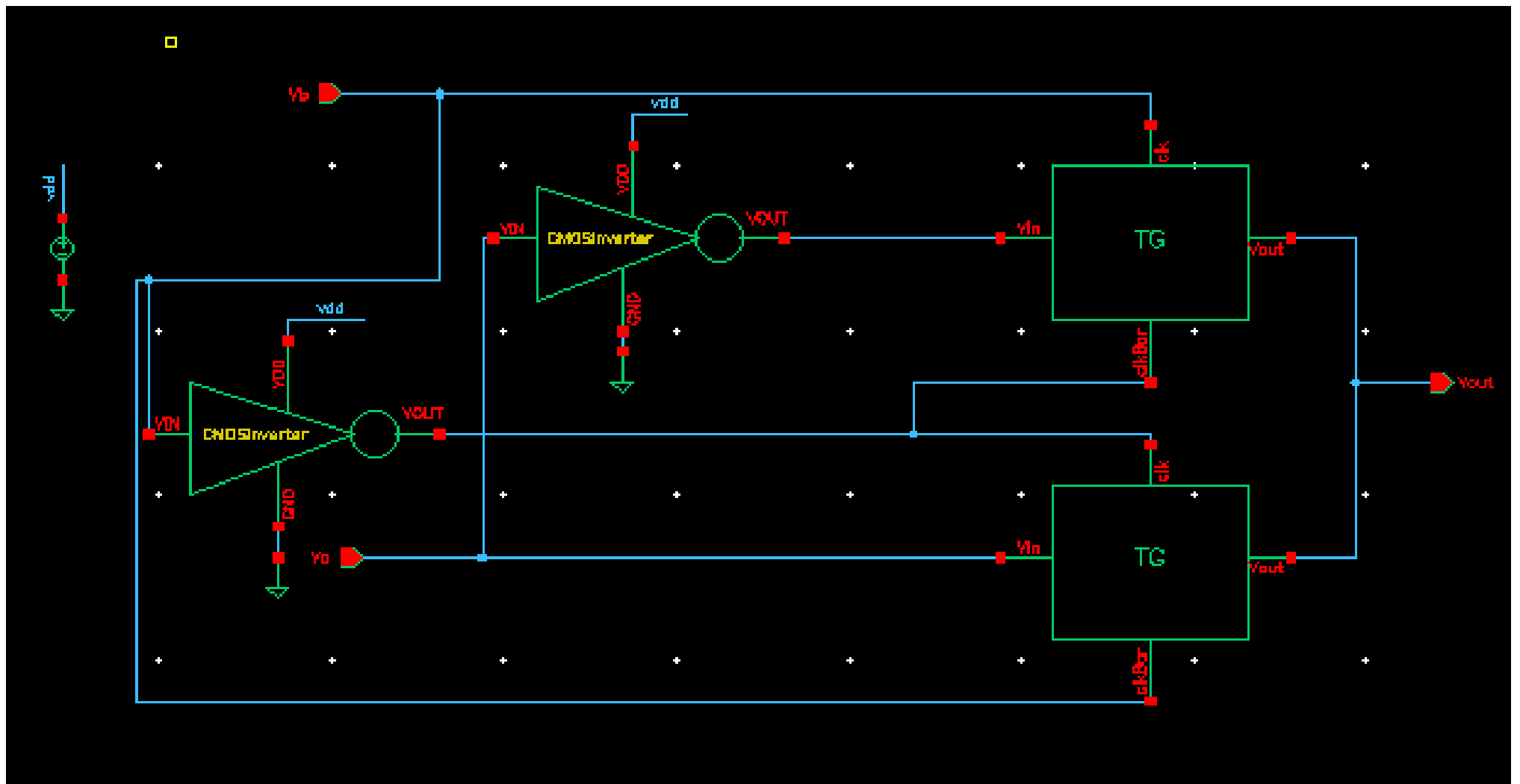
## XOR Schematic



- To achieve the optimal implementation of the XOR functionality in terms of delay time, we utilized Transmission Gate Logic (TGL) for the XOR gate.



## 4.6 XOR Symbol

 


## XOR Testbench

  
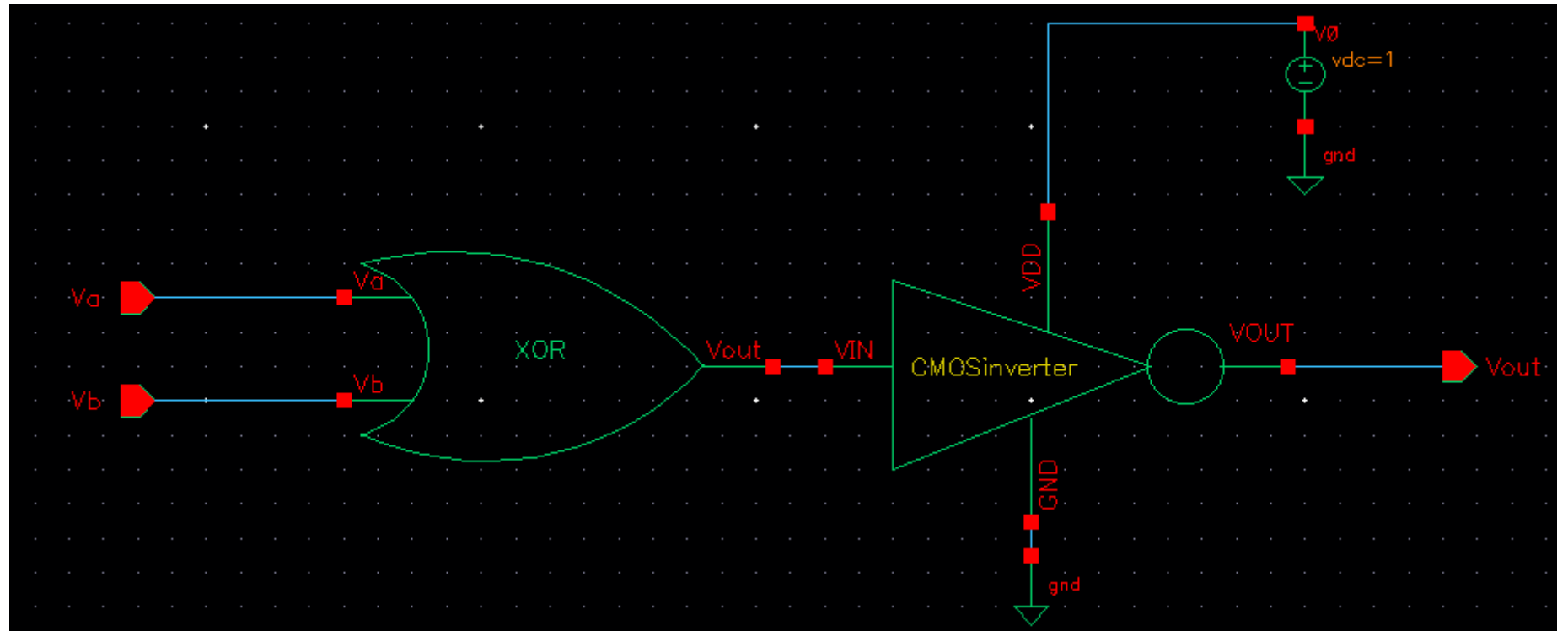
## 4.8 XNOR Schematic


---

- To ensure the most optimal implementation of the XNOR functionality in terms of delay time, we employed Transmission Gate Logic (TGL) for the XNOR gate.




## 4.2 XNOR Symbol

---

 

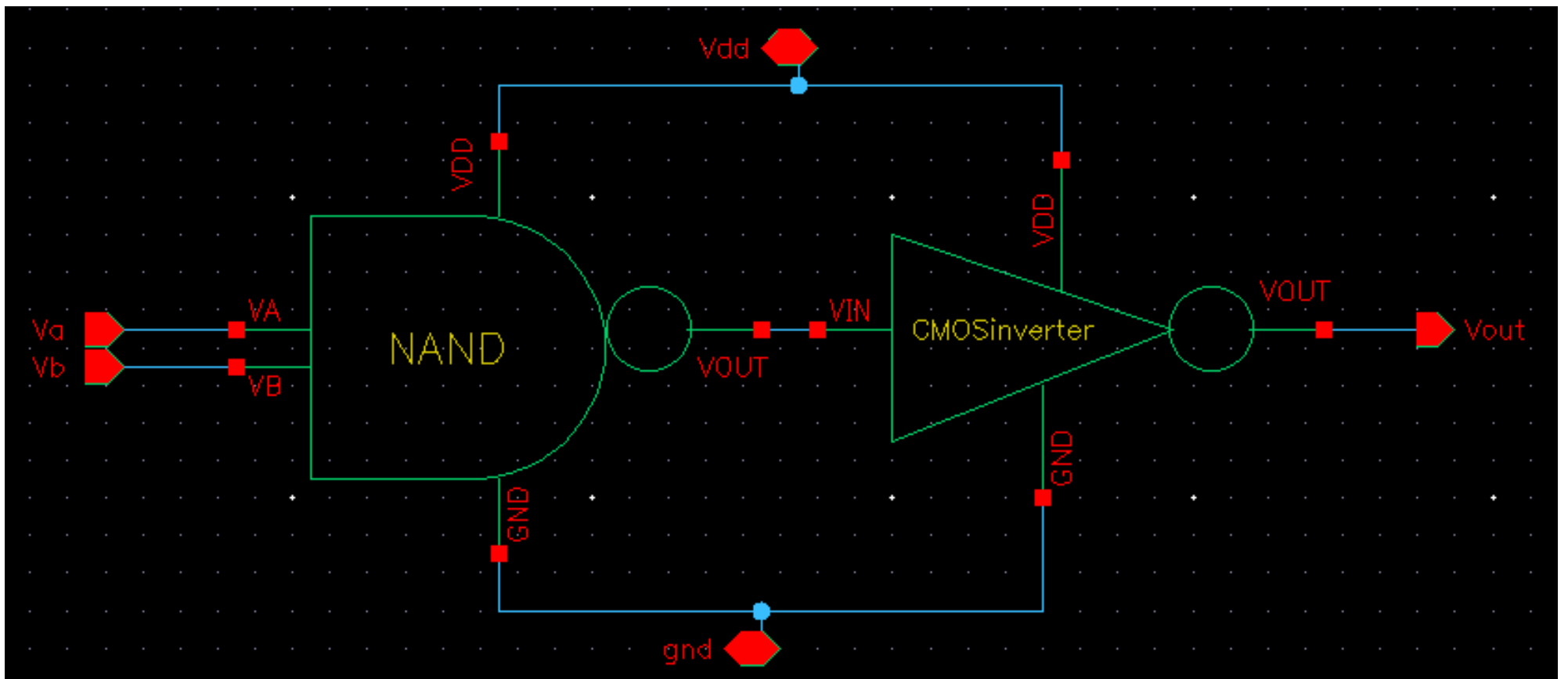
## 4.3 AND Schematic



- By utilizing the NAND and NOR gates we have implemented, we can easily obtain the AND and OR functionality by incorporating an inverter after each respective gate. Additionally, the buffer functionality is achieved by employing a sequence of two inverters.



## 4.9 AND Symbol

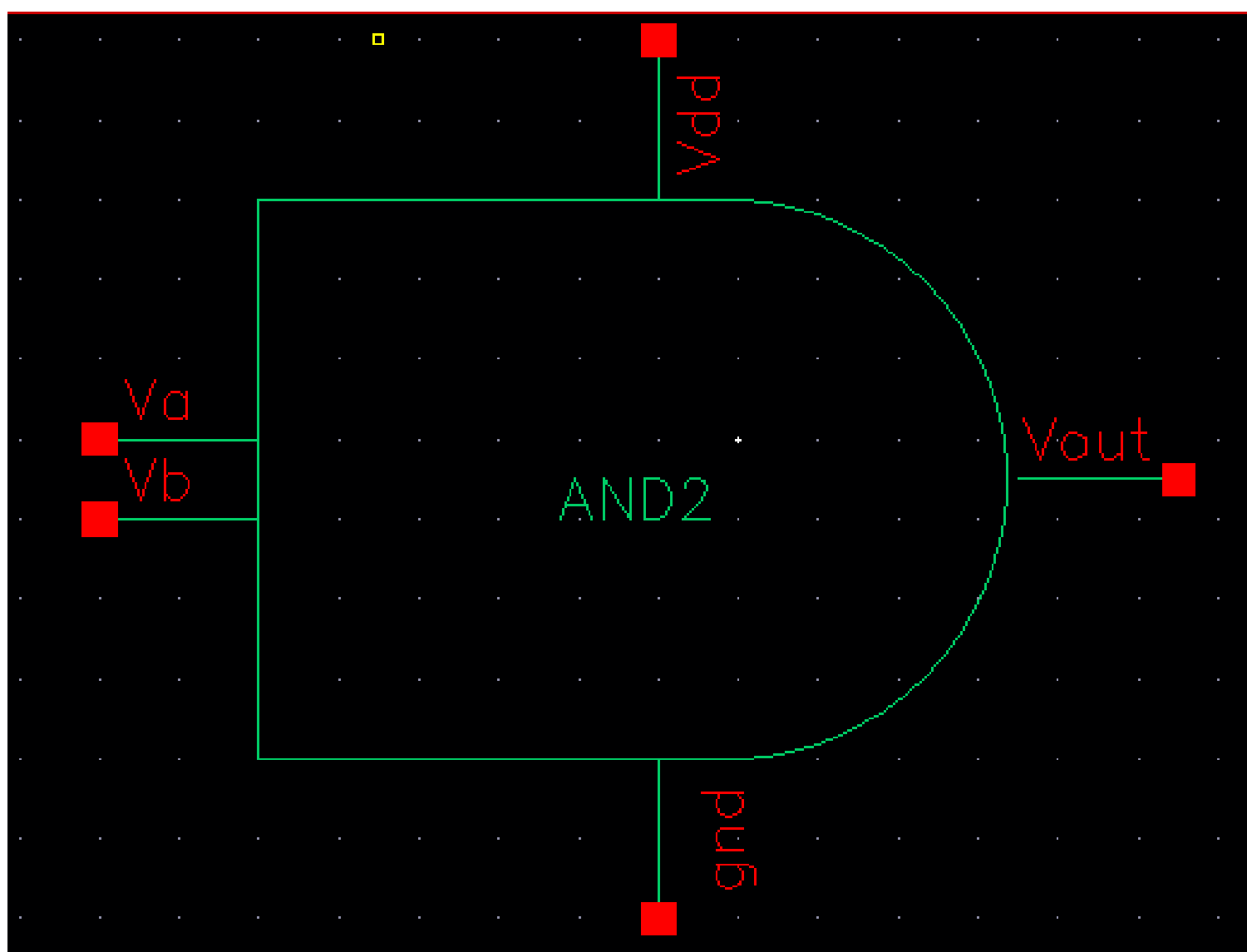


## 4.1 AND Testbench

 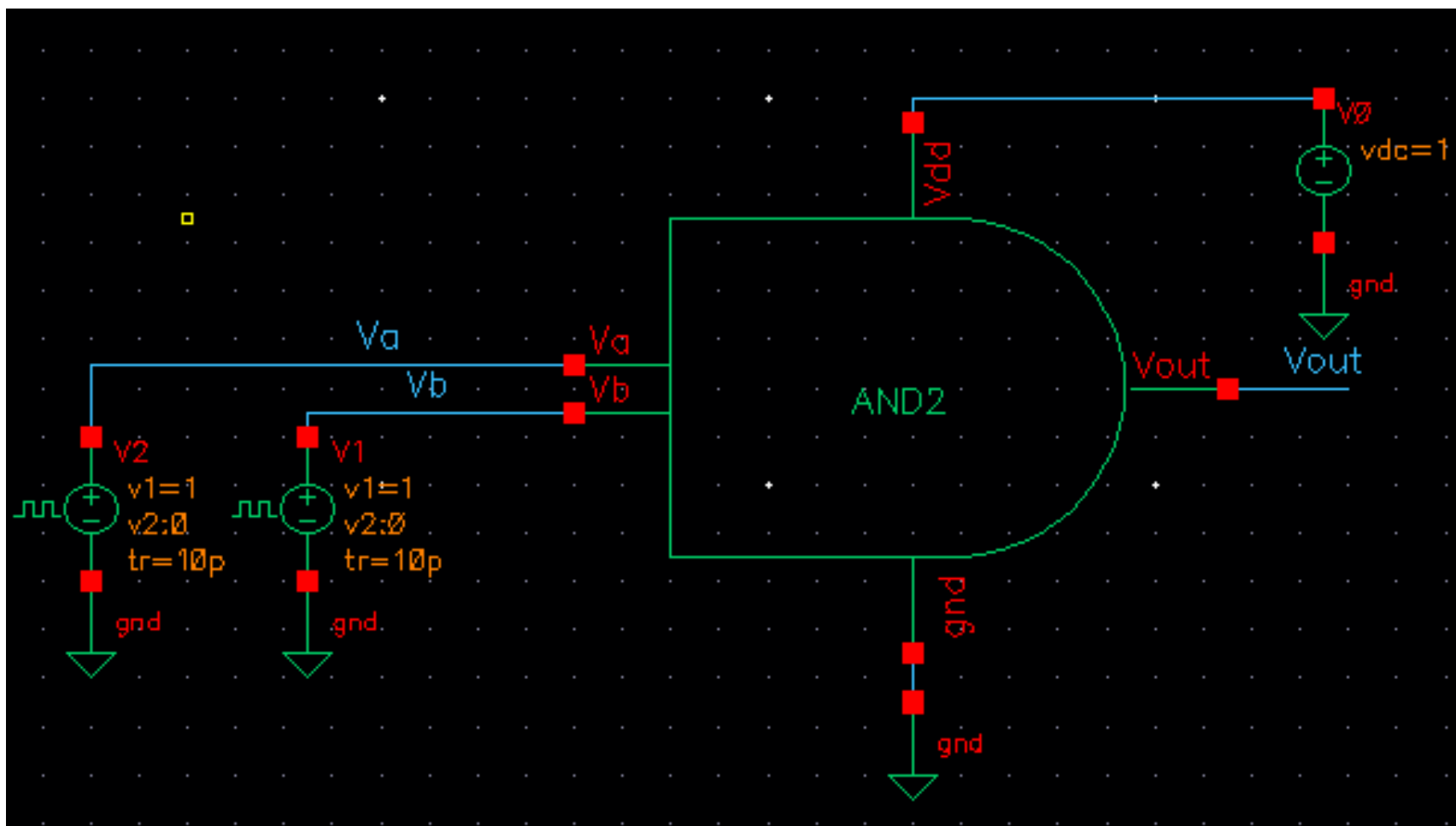


So:  $T_{pd} = 14.68 \text{ ps}$





## 4.2 OR Schematic

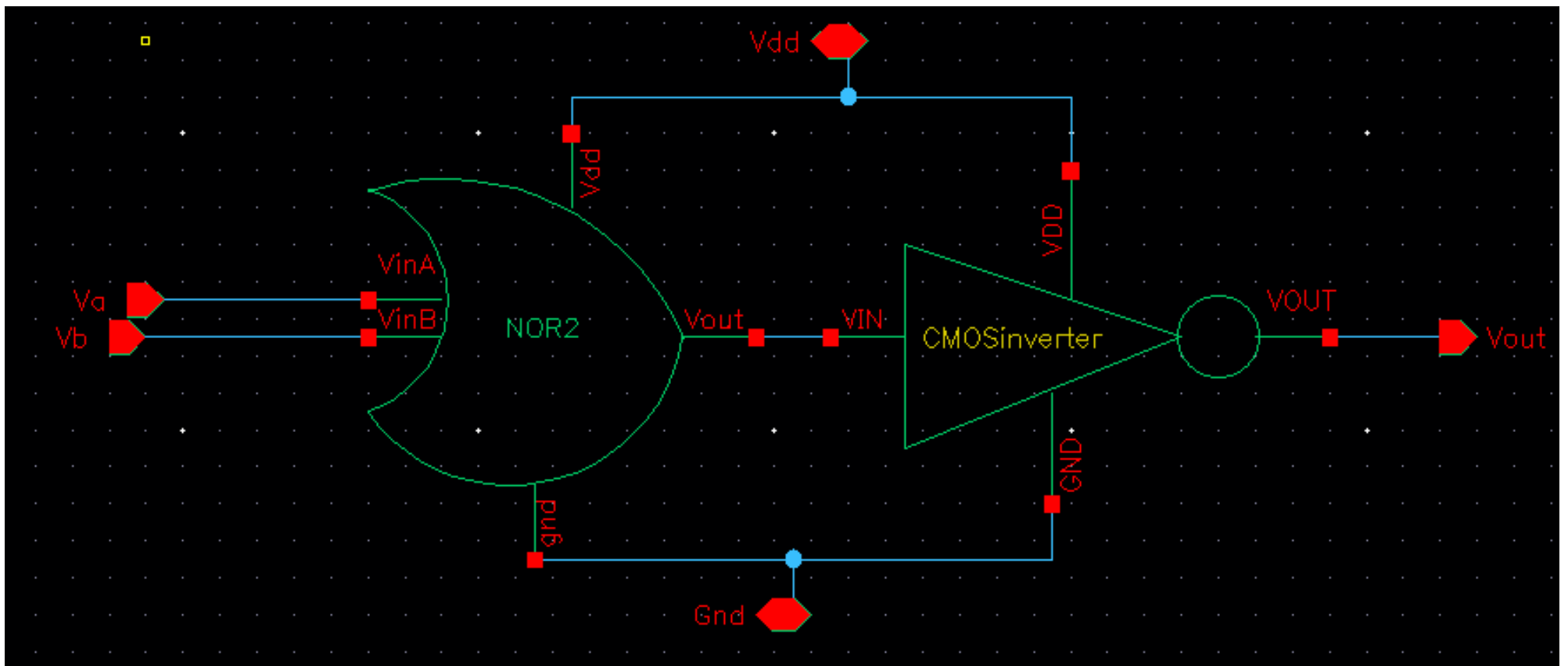

## 4.4 OR Symbol

 


## 4.1 OR Testbench

 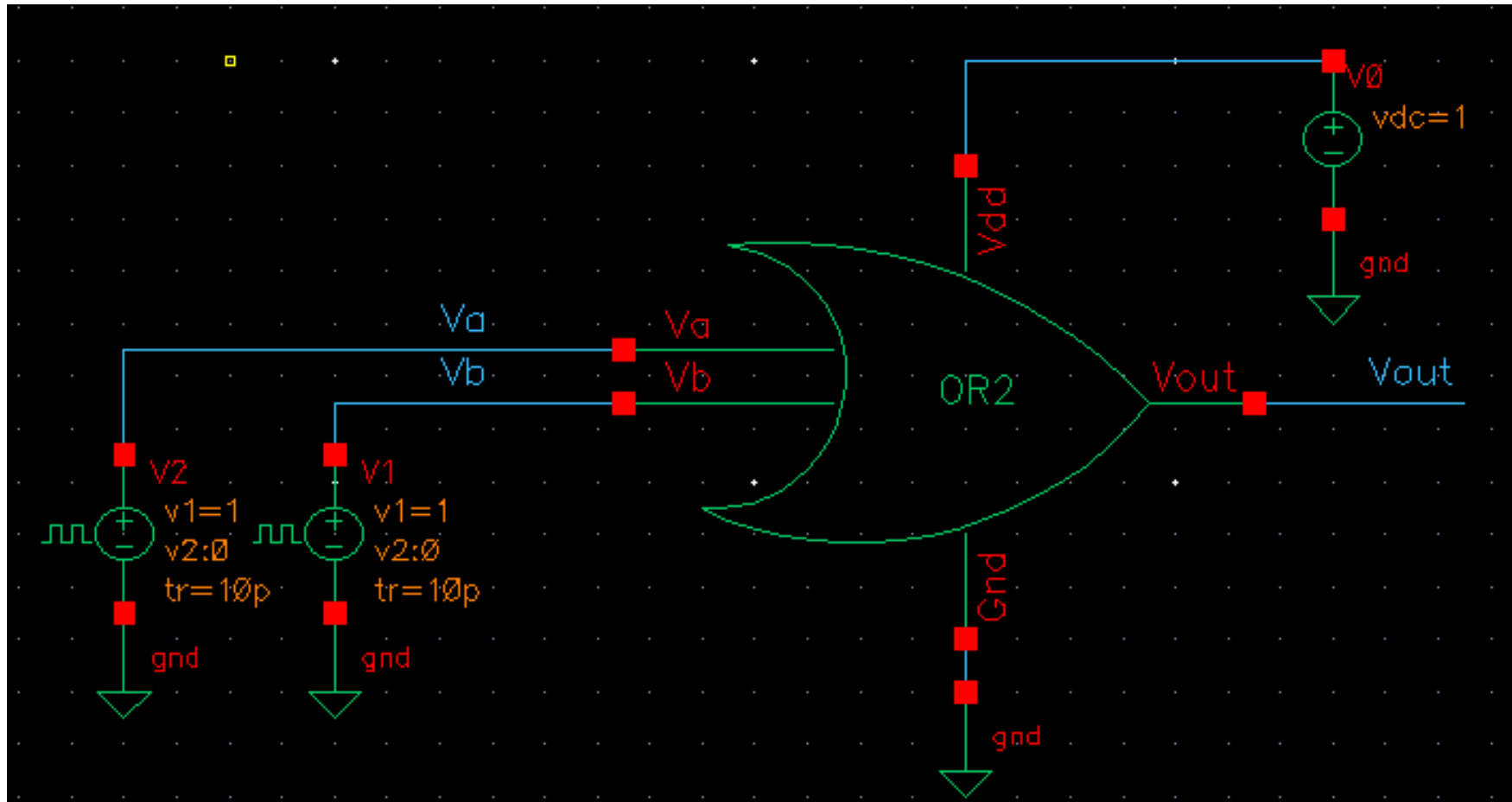


So:  $T_{pd} = 18.1 \text{ ps}$



## 4.5 Buffer Schematic

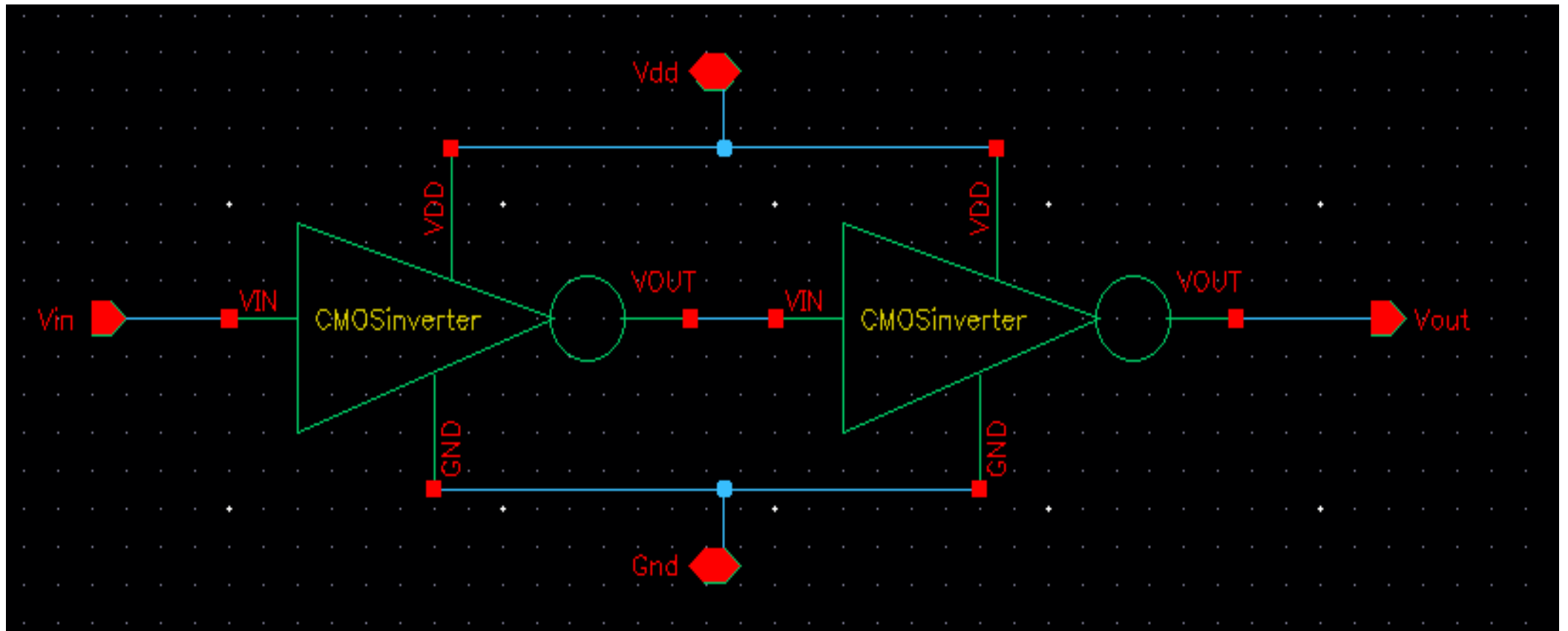

## 4.2 Buffer Symbol

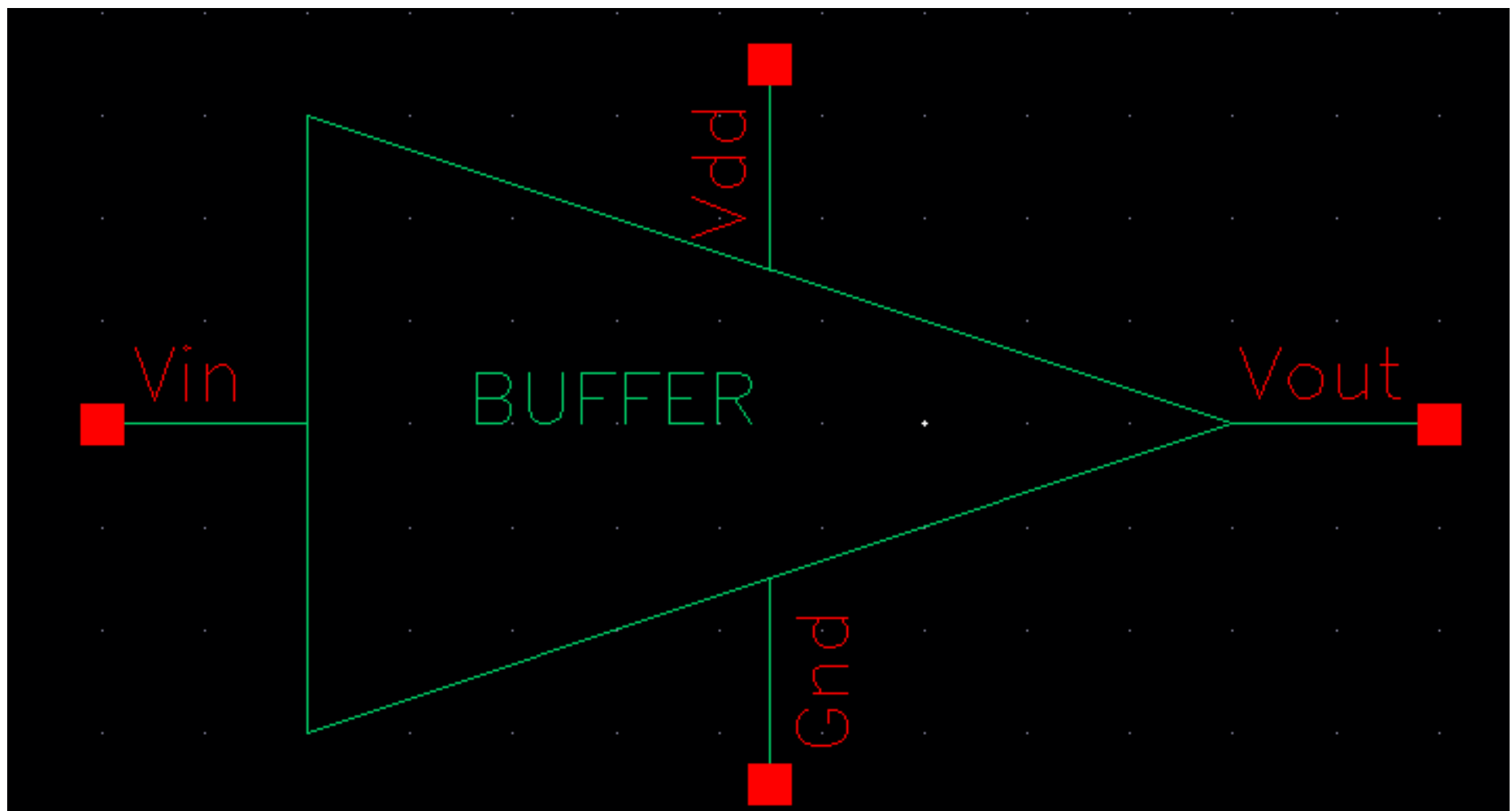

# Buffer Testbench

 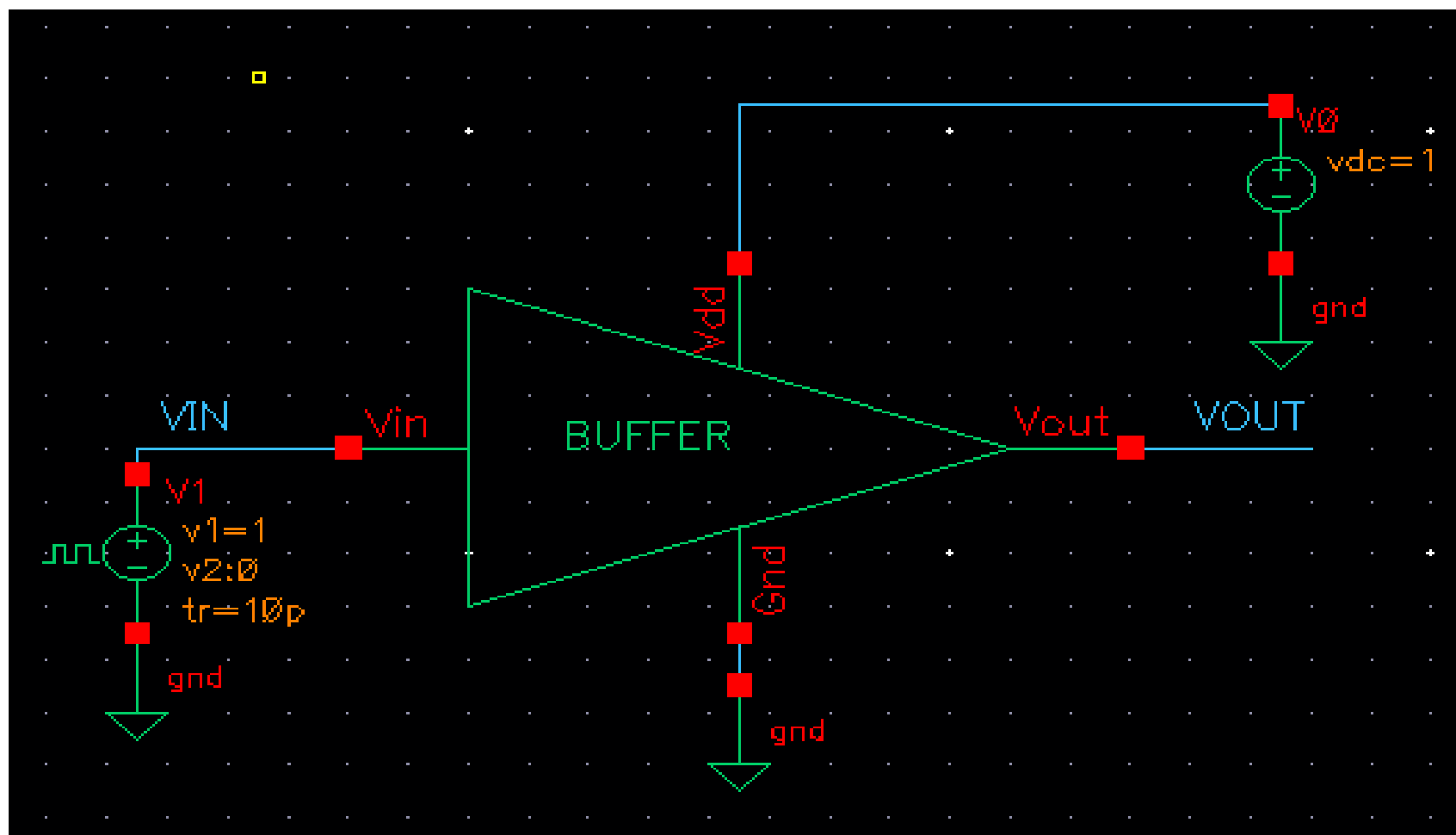

So:  $T_{pd} = 13.74 \text{ ps}$


## 4.1 MUX 2x1 Schematic

- To enable the selection of various options, it is necessary to design a multiplexer (MUX) with different configurations such as 2x1, 4x1, or 8x1. To accomplish this, we begin by designing the fundamental building block, which is the 2x1 MUX.
- (TG Multiplexer) is the most efficient one
- The truth table corresponding to the 2x1 MUX is as follow

### 2-to-1 Multiplexer



S	I <sub>0</sub>	I <sub>1</sub>	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Truth table for 2x1 MUX

 


S	Y
0	I <sub>0</sub>
1	I <sub>1</sub>



Condensed Truth Table

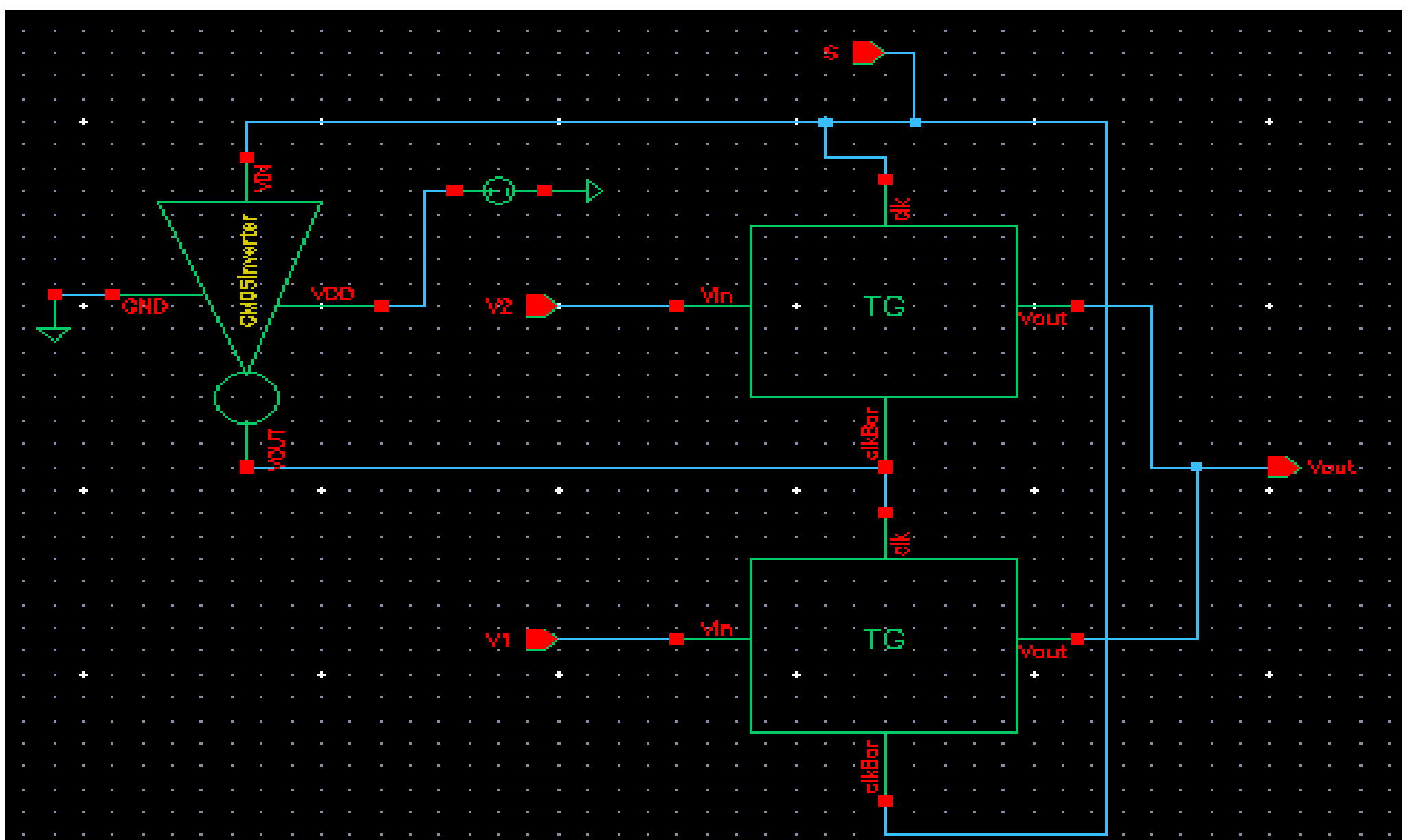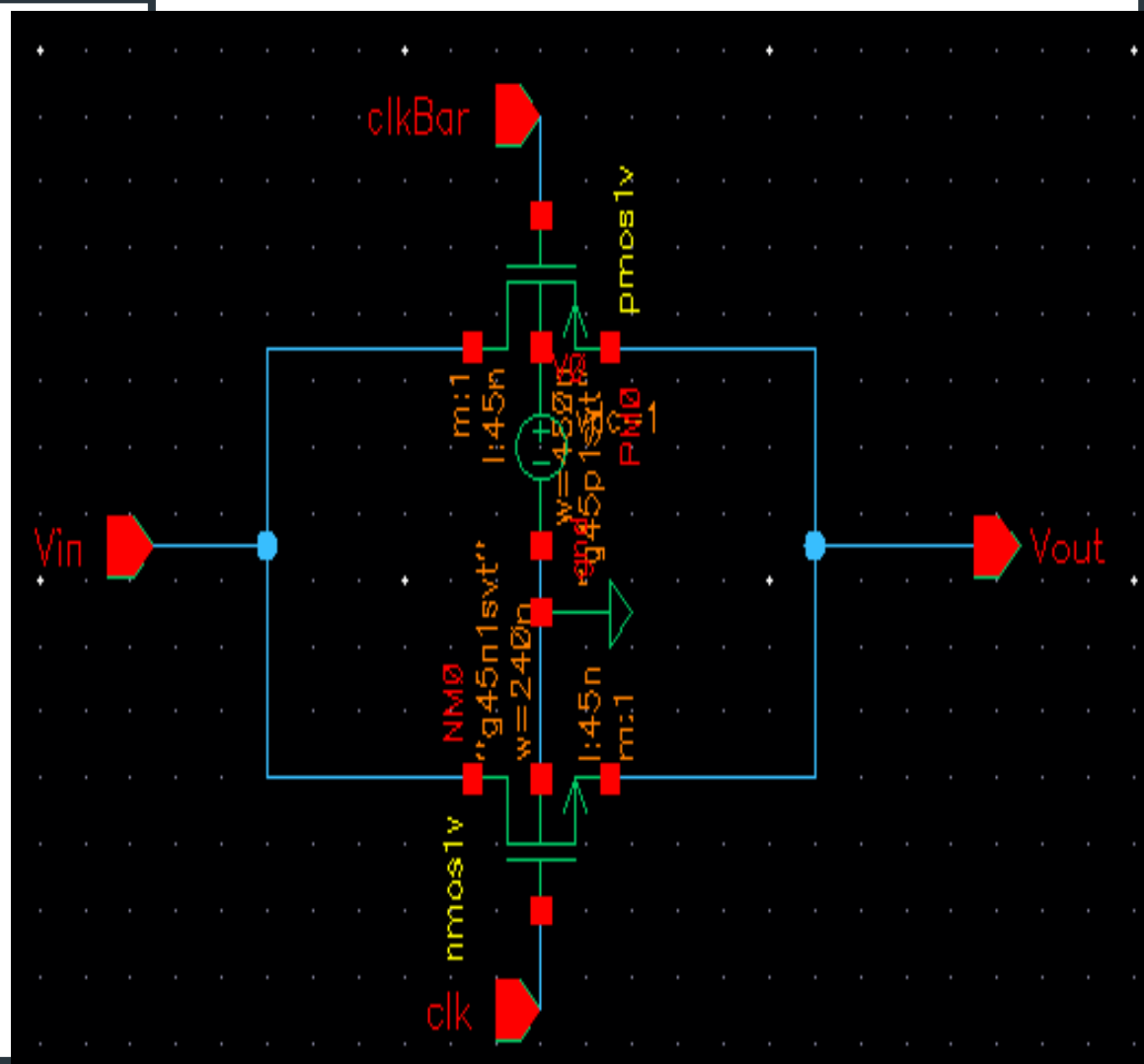

# MUX 2x1 Symbol

 


# MUX 2x1 Testbench

 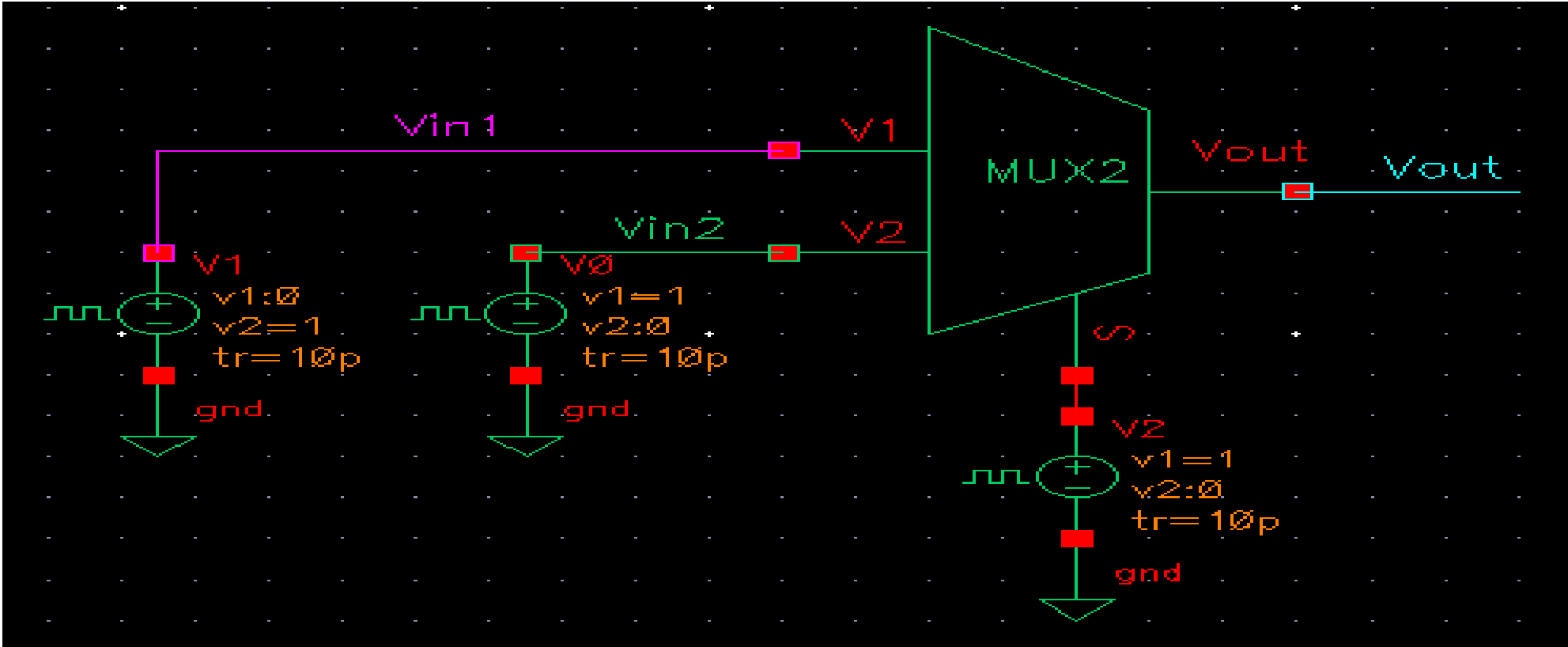

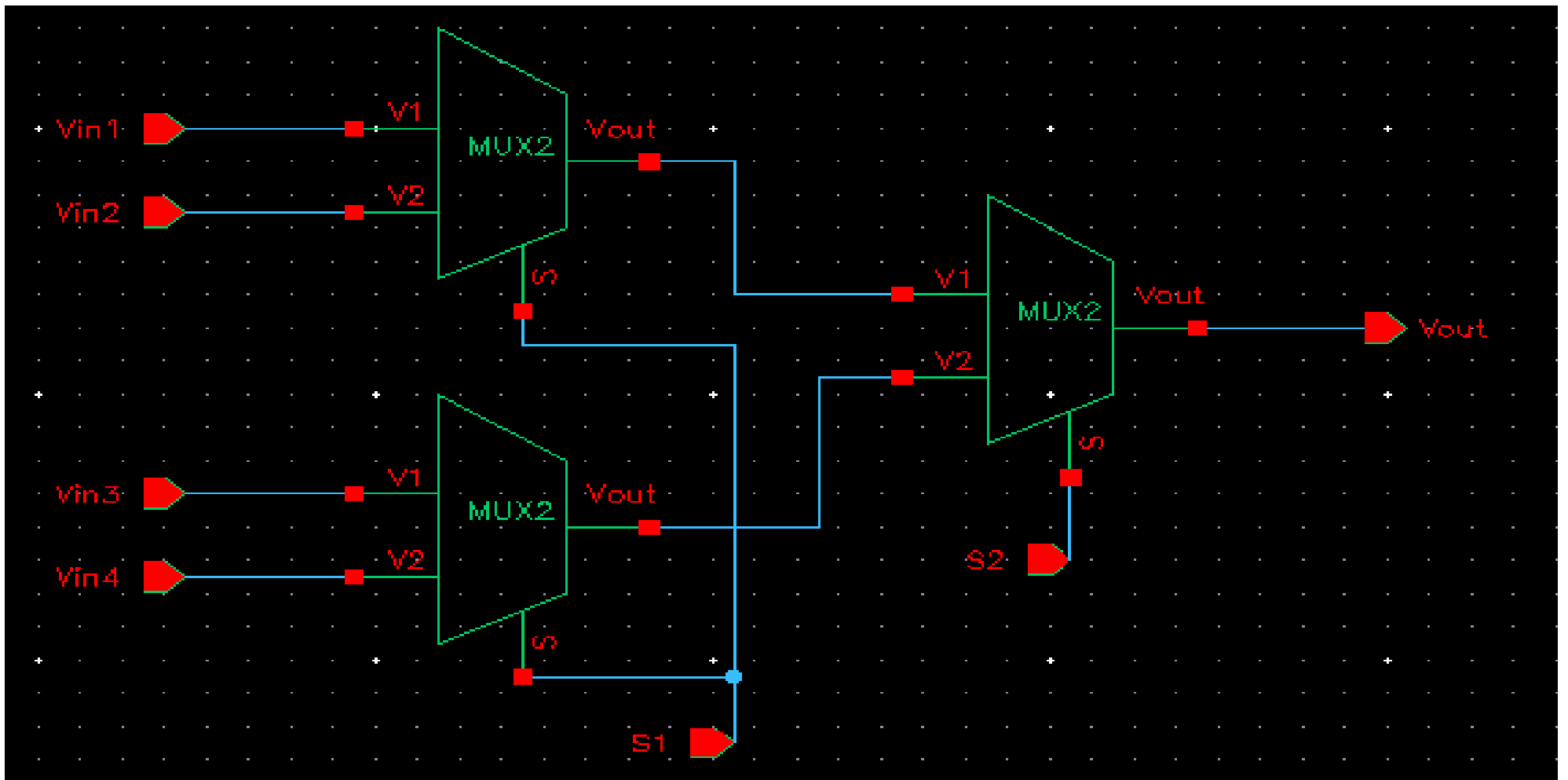
## 4.2 MUX 4x1 Schematic


- Having established the foundational building block, we can now proceed to design larger multiplexers (MUXs) with expanded input options. By utilizing the 2x1 MUX as a building block, we can construct MUXs of various sizes, such as 4x1, 8x1, and beyond, to cater to our specific needs and requirements.



## 4.6 MUX 4x1 Symbol

 

## 4.1 MUX 4x1 Testbench

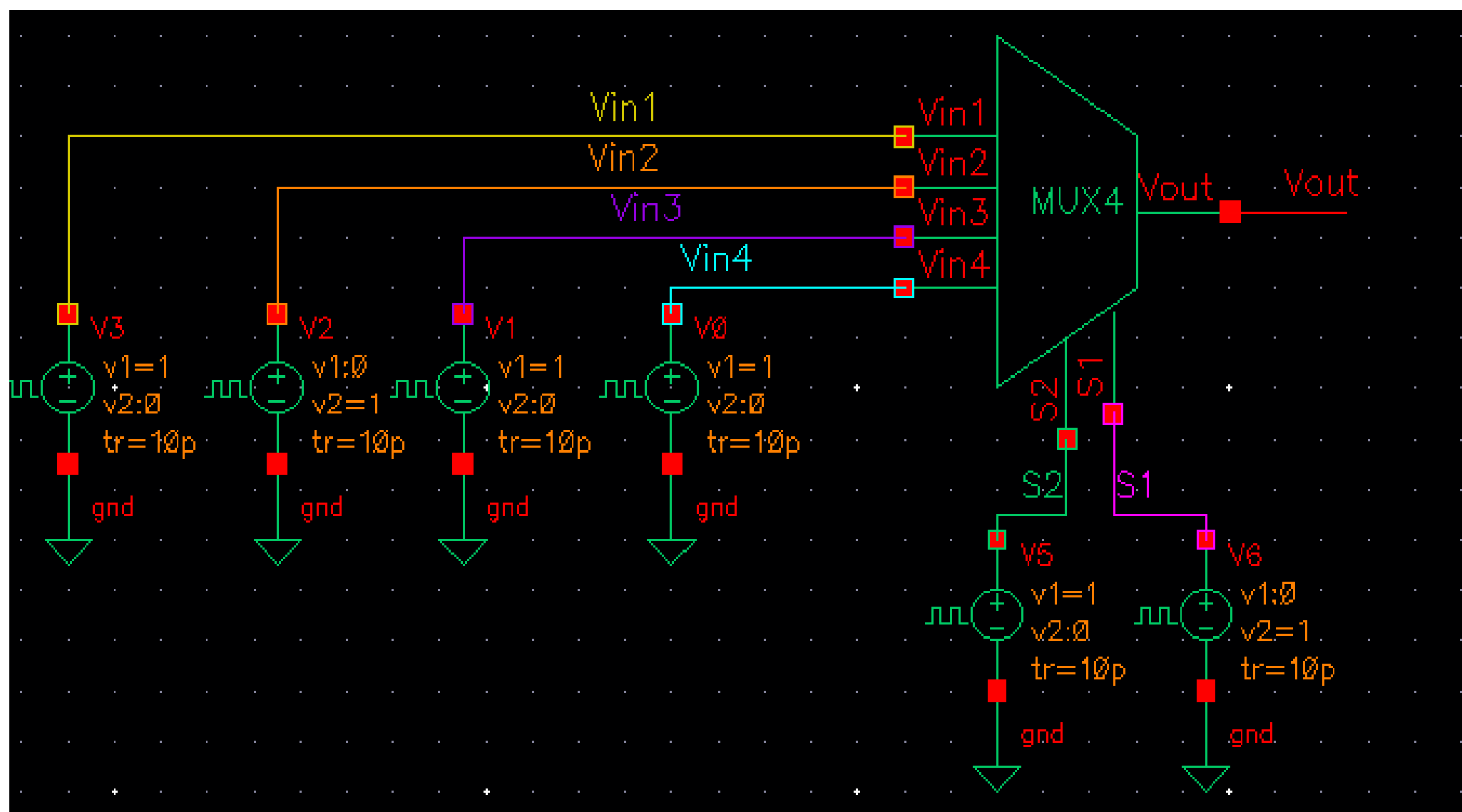


HEY MUX4\_test schematic x

Transient


Sat Sep 28 06:50:50

1

 







# 4.2 MUX 8x1 Schematic

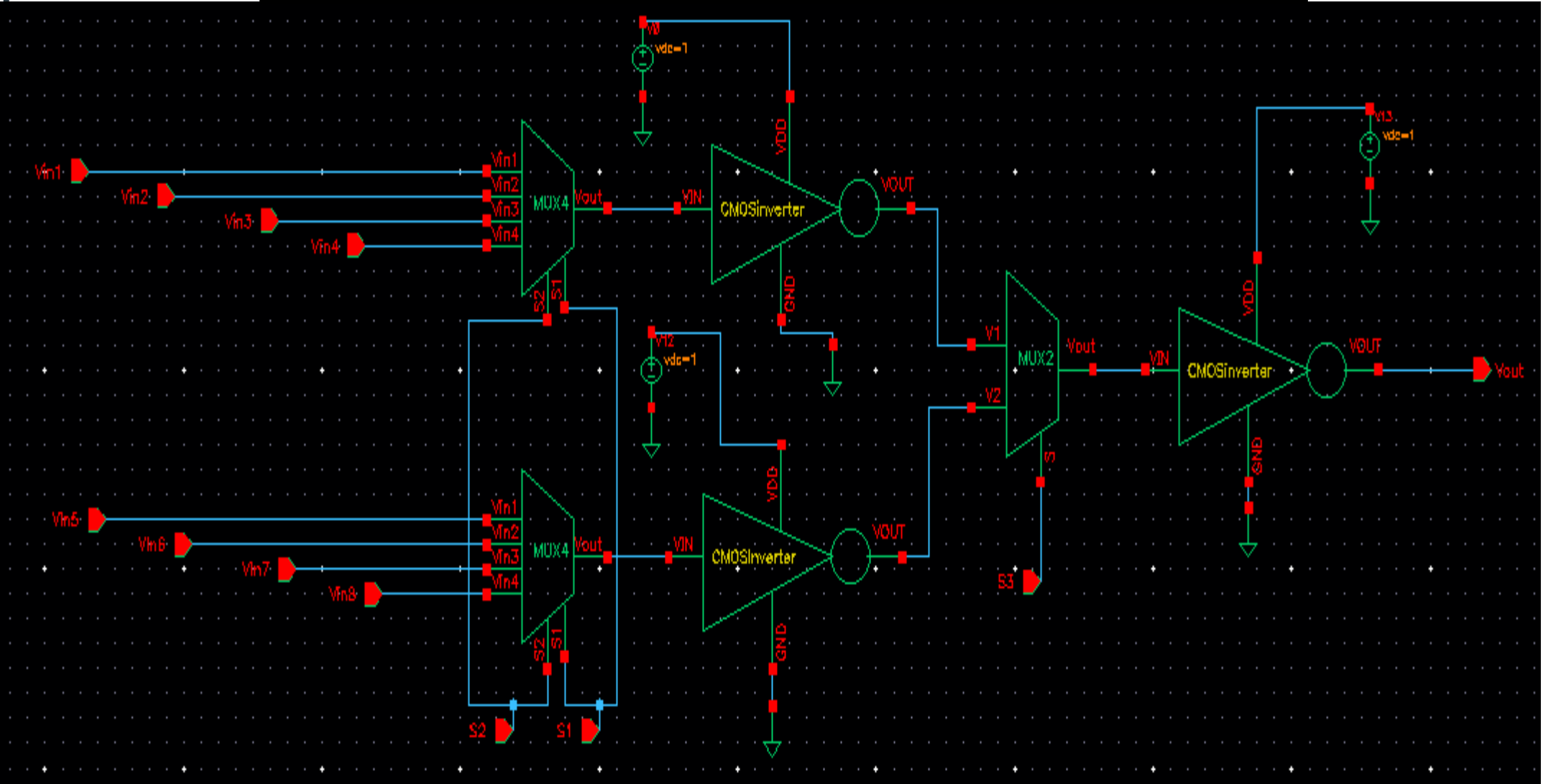



# 4.3 MUX 8x1 Symbol



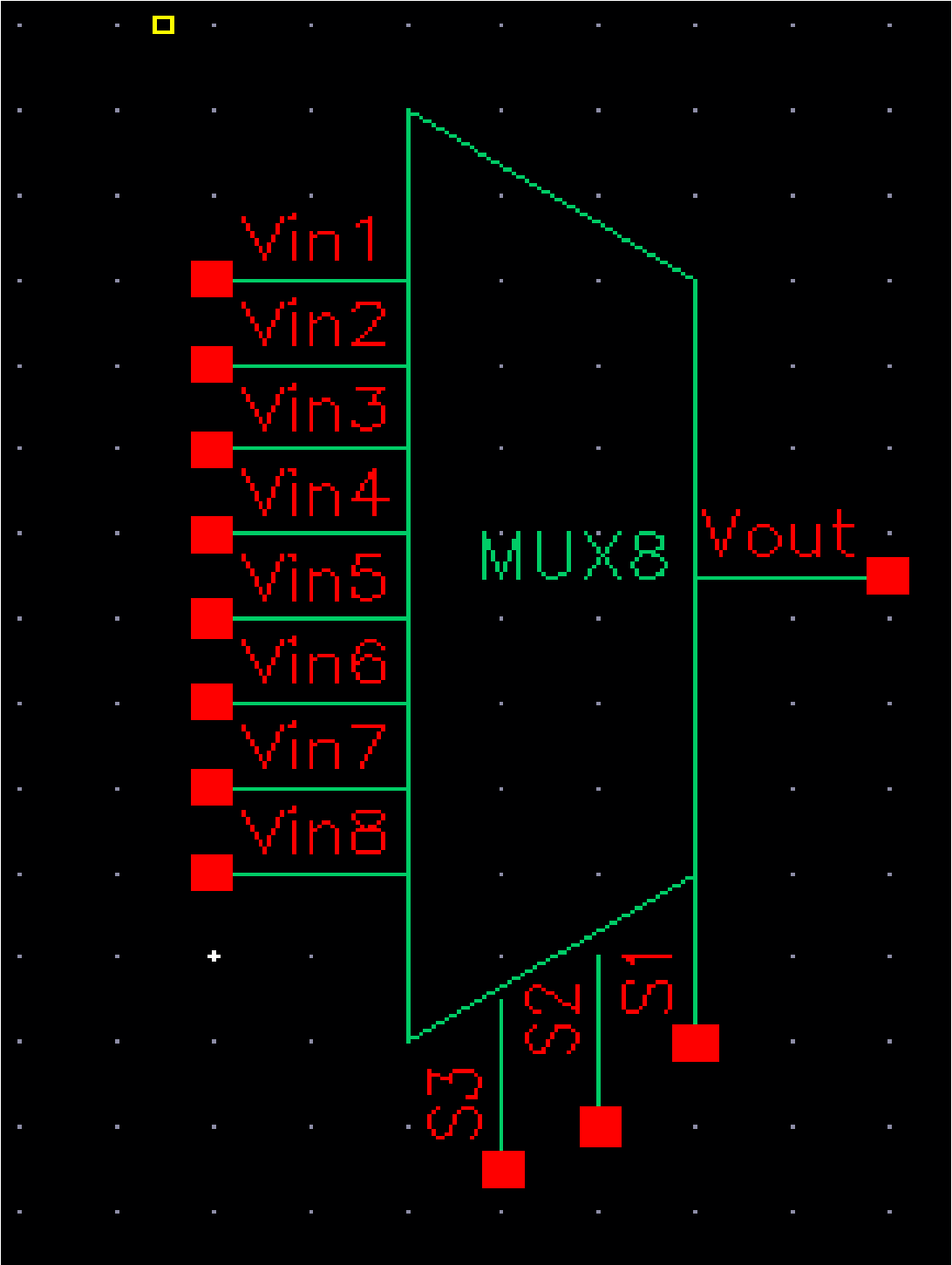




# MUX 8x1 Testbench

 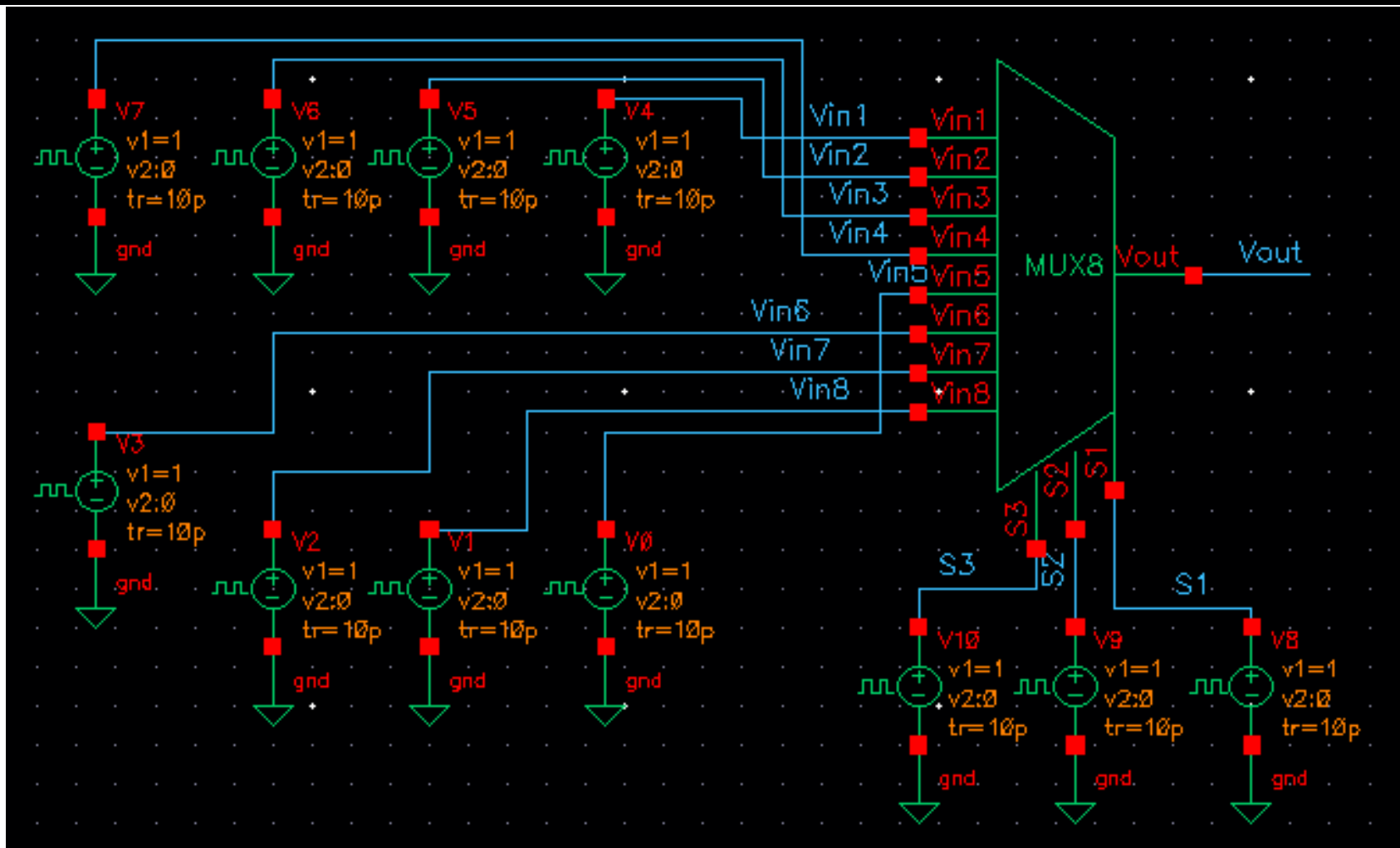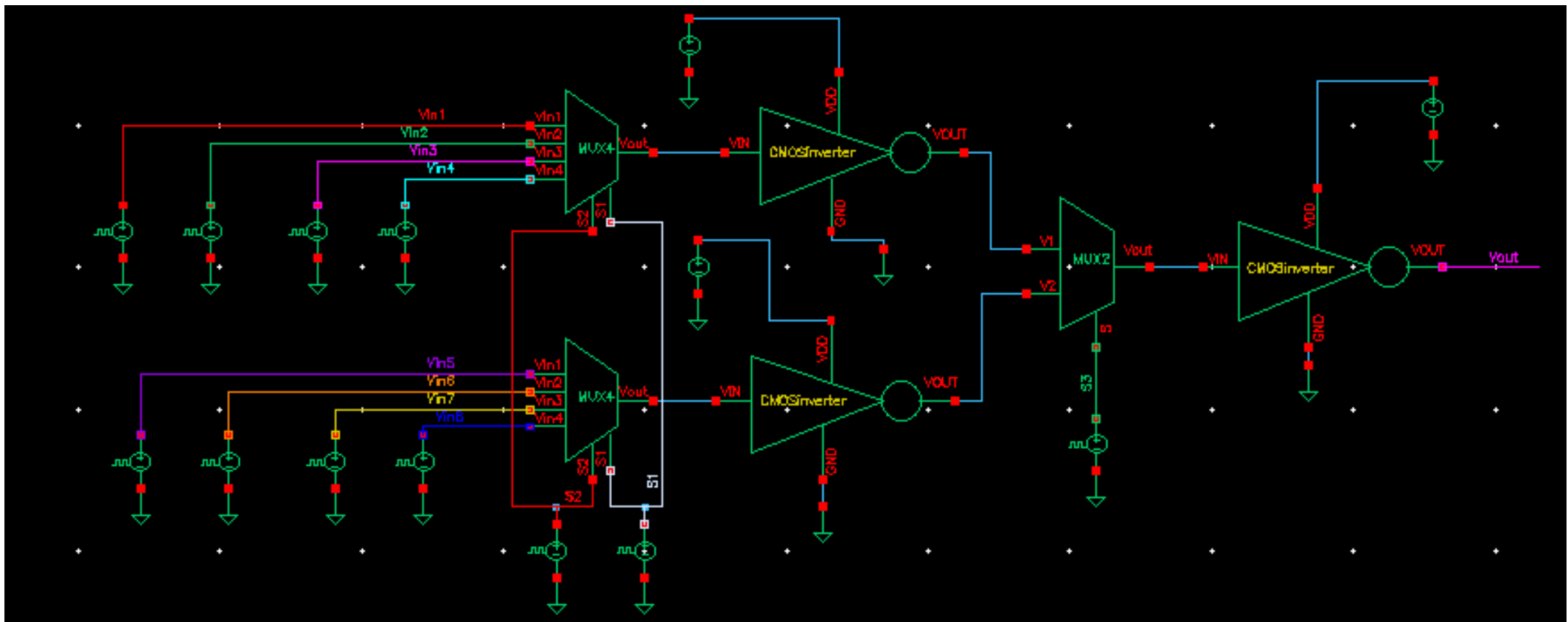


# Flip Flops Schematic

 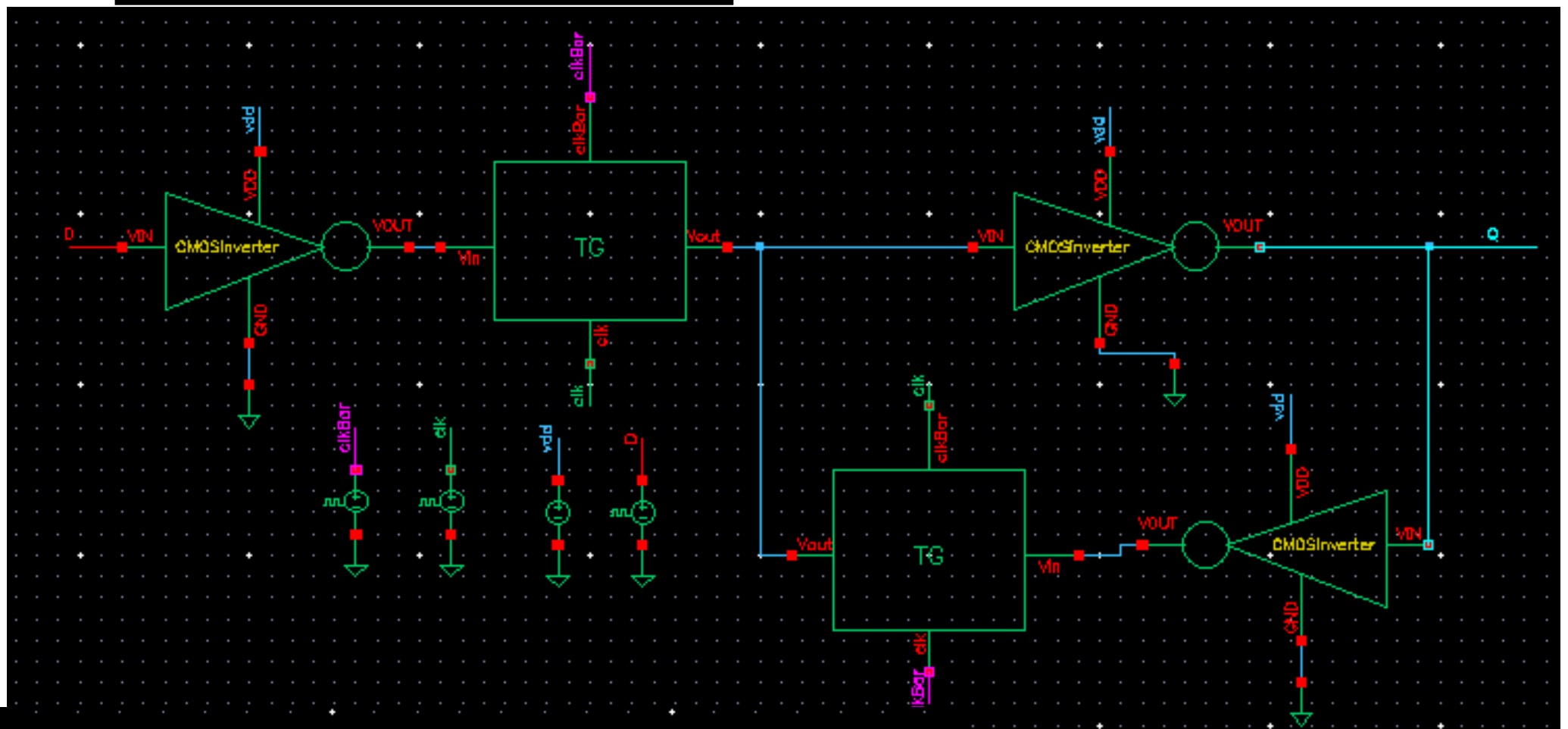

  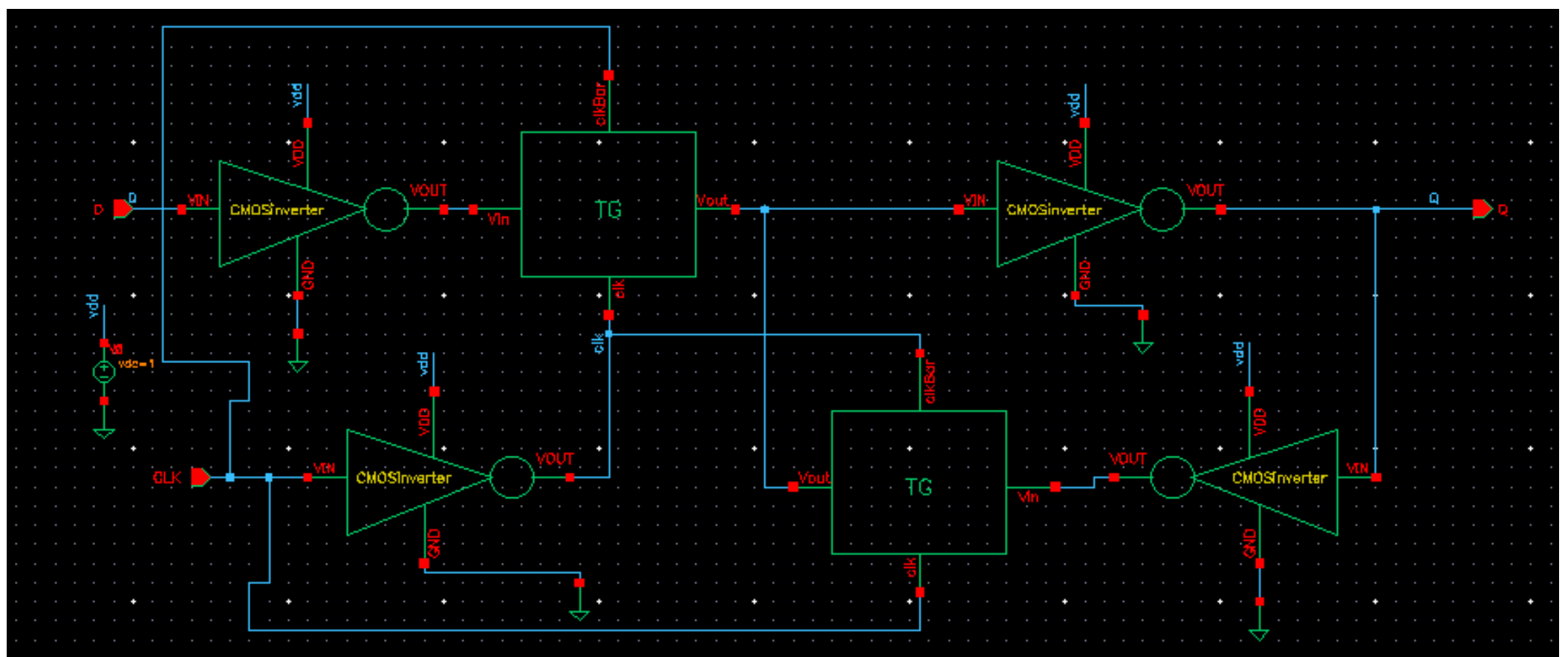


 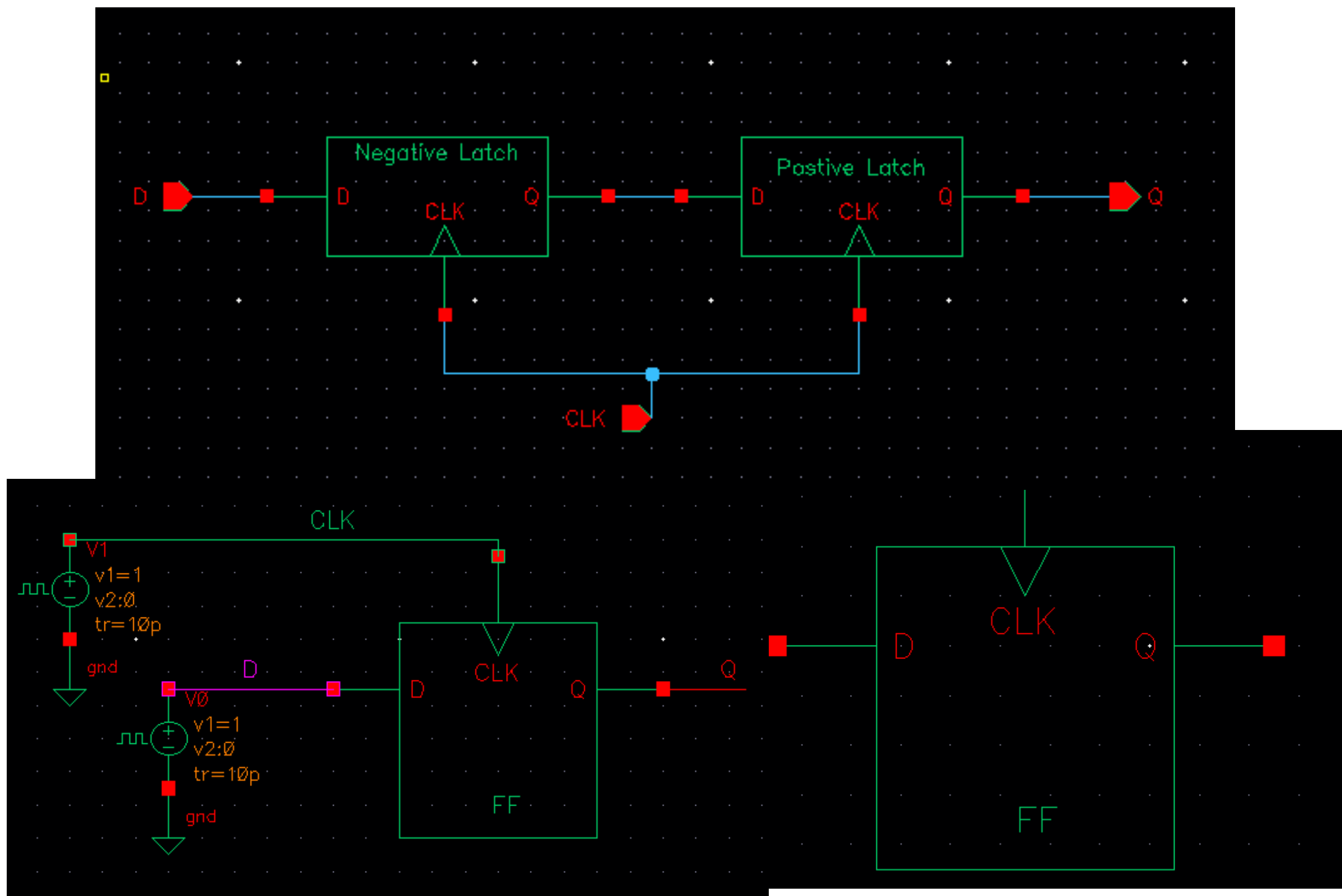

## 4.3 Full Adder Schematic

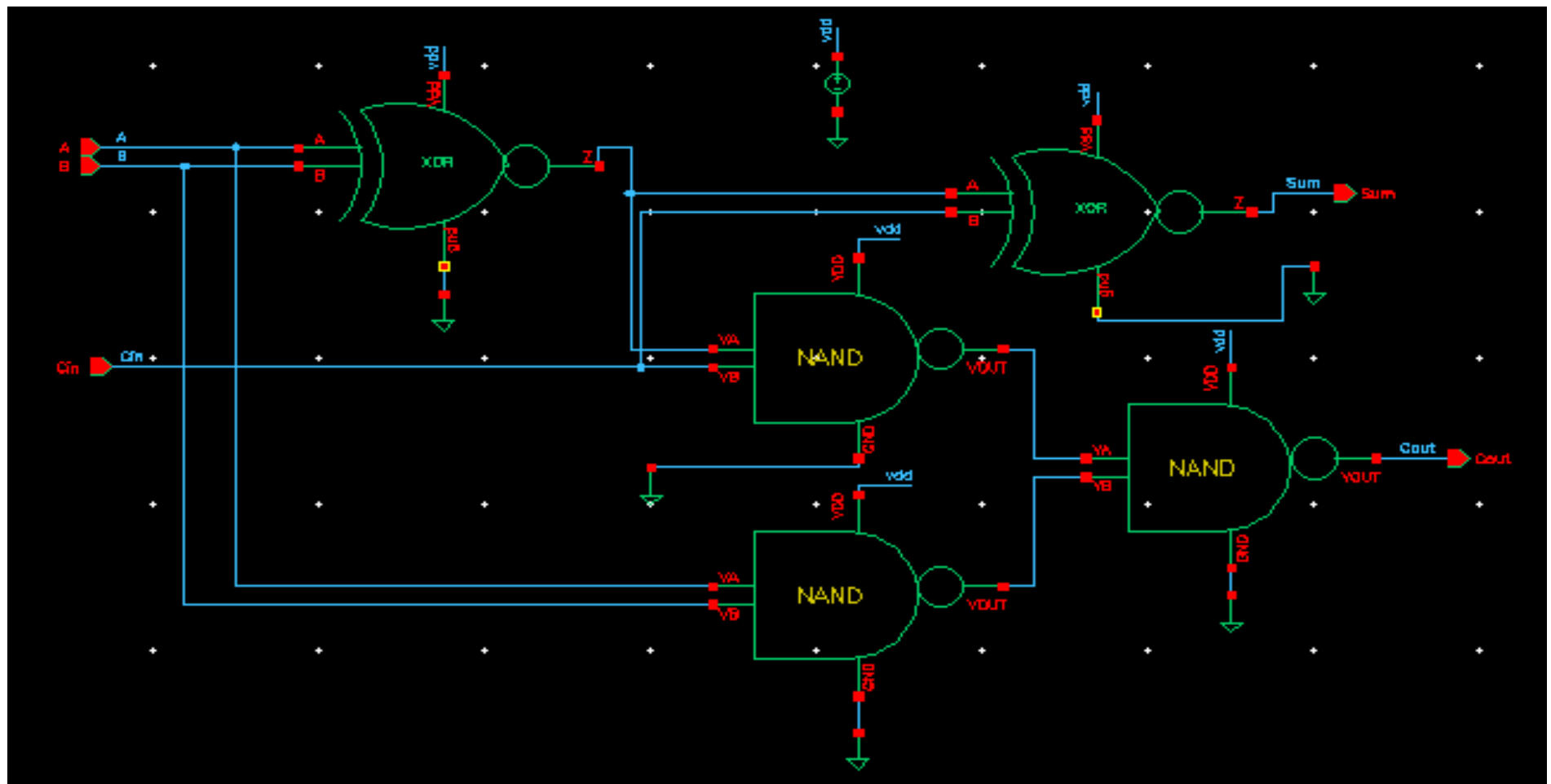


## 4.4 Full Adder Symbol

 
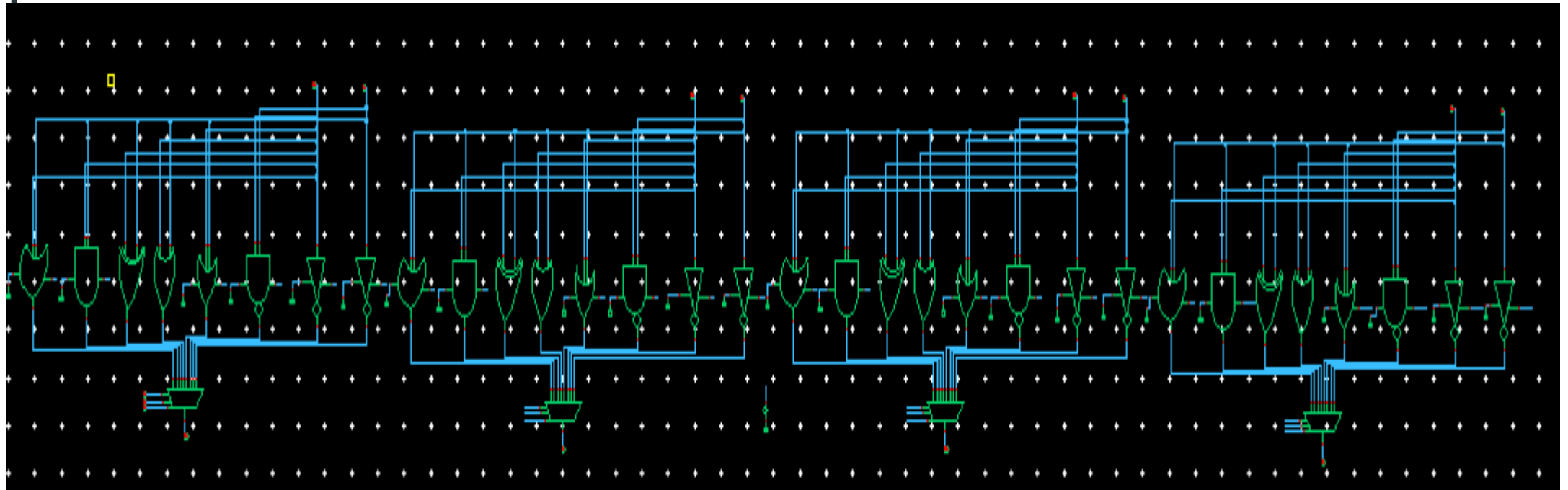
## 4.5 Logic Unit Schematic


---

- With all the essential components and building blocks at our disposal, we can proceed to construct the complete Arithmetic Logic Unit (ALU), which comprises two primary blocks: the Logic Unit and the Arithmetic Unit. Our initial focus will be on building the Logic Unit.




## 4.4 Logic Unit Symbol

---

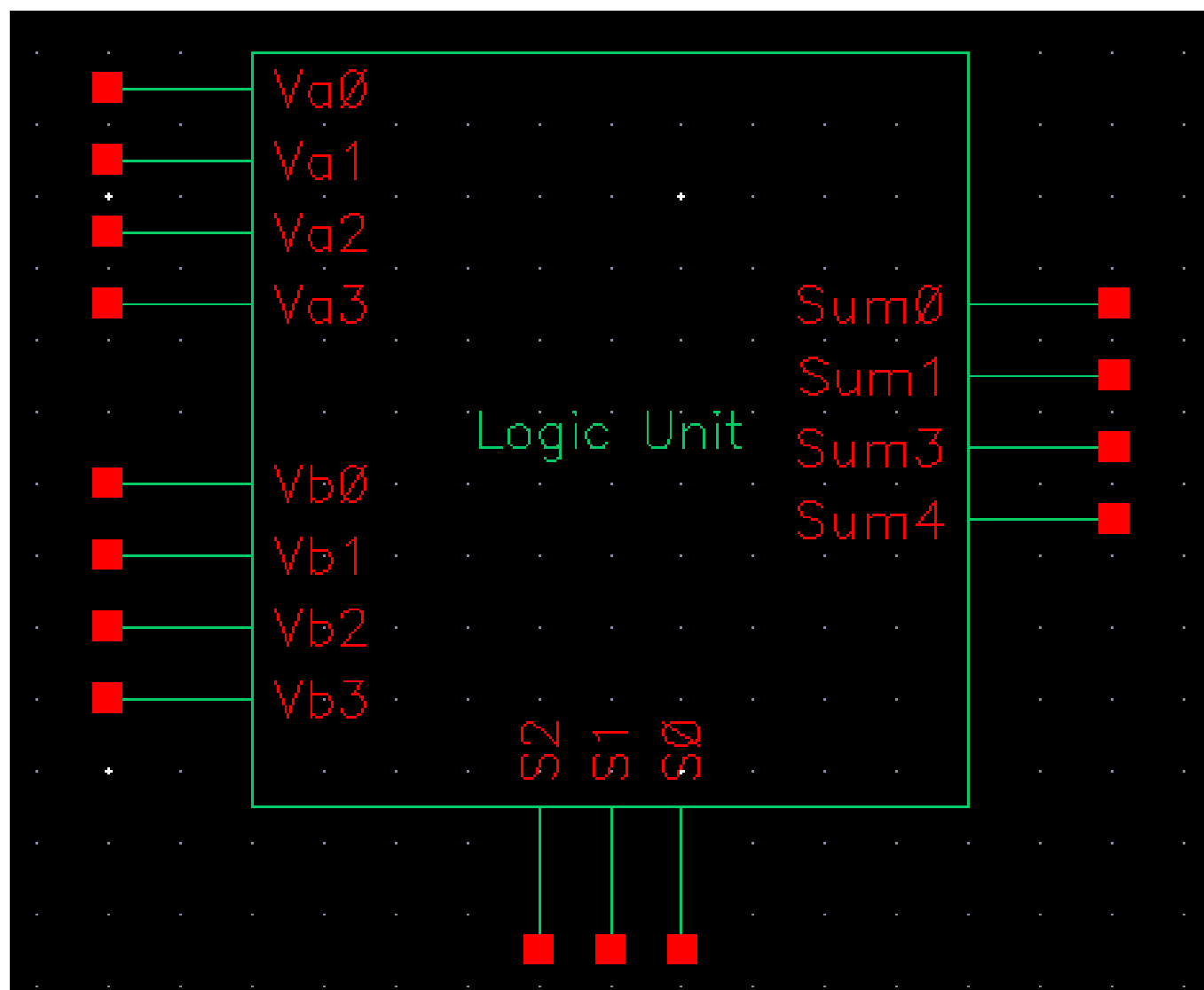

# 4.1 Logic Unit Testbench

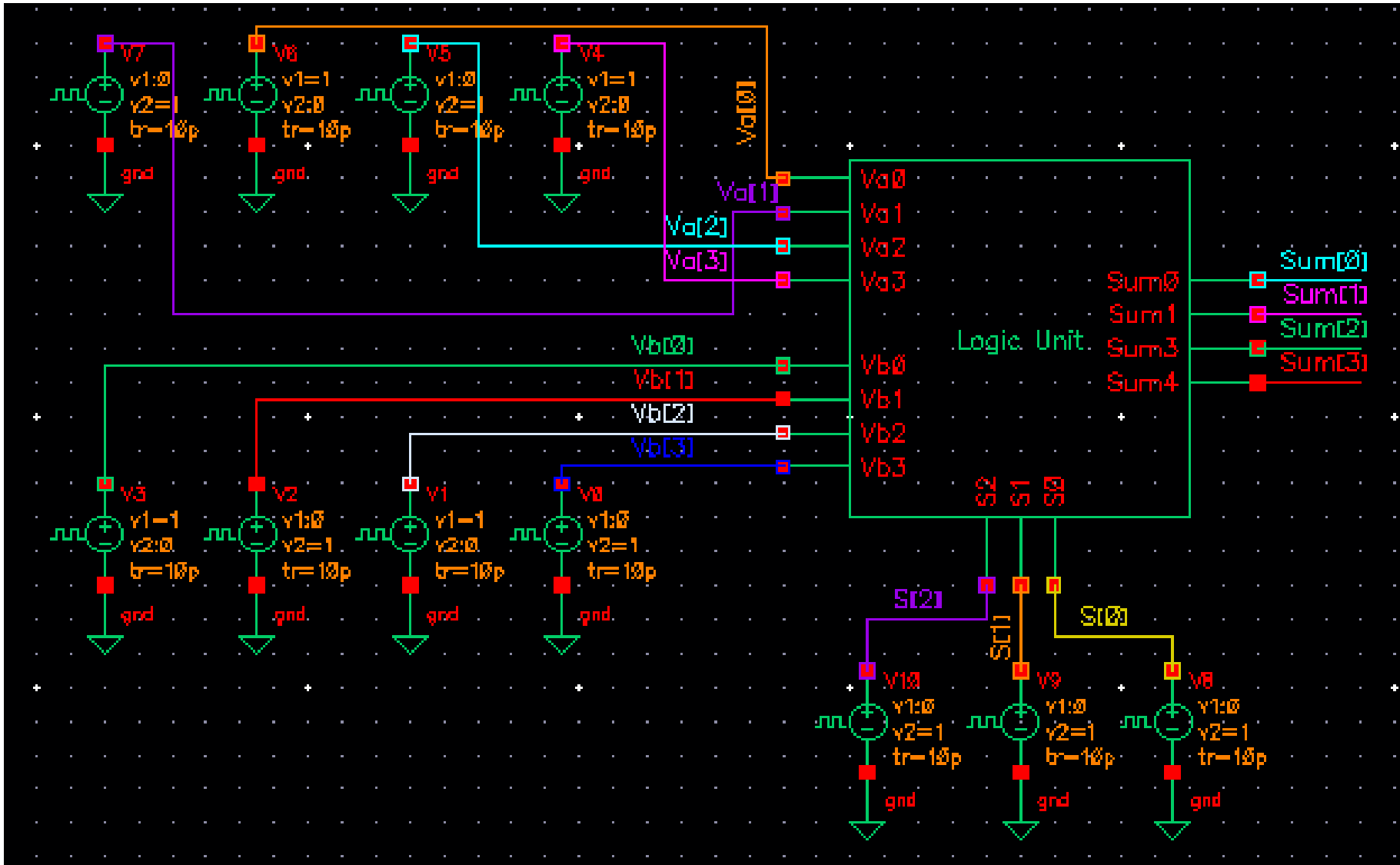


Outputs				
Name/Signal/Expr	Value	Plot	Save	Save Options
1 Va[0]		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
2 Va[1]		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
3 Va[2]		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
4 Va[3]		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
5 Vb[0]		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
6 Vb[1]		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
7 Vb[2]		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
8 Vb[3]		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
9 S[0]		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
10 S[1]		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
11 S[2]		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
12 Sum[0]		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
13 Sum[1]		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
14 Sum[2]		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
15 Sum[3]		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv


Plot after simulation: Auto Plotting mode Replace




 
Testcase:  $Va = 0110, Vb = 1010, S = 111, Result = 0001$




 
Testcase:  $Va = 1001, Vb = 0101, S = 100, Result = 1100$



  
Testcase:  $Va = 0110, Vb = 1010, S = 001, Result = 0101$



  
Testcase:  $Va = 1001, Vb = 0101, S = 010, Result = 1110$



 Testcase:  $Va = 0100, Vb = 1001, S = 111, Result = 0010$




 Testcase:  $Va = 1011, Vb = 0110, S = 011, Result = 1111$






 Testcase:  $Va = 1011, Vb = 0110, S = 001, Result = 1001$





 Testcase:  $Va = 0100, Vb = 1001, S = 100, Result = 1101$



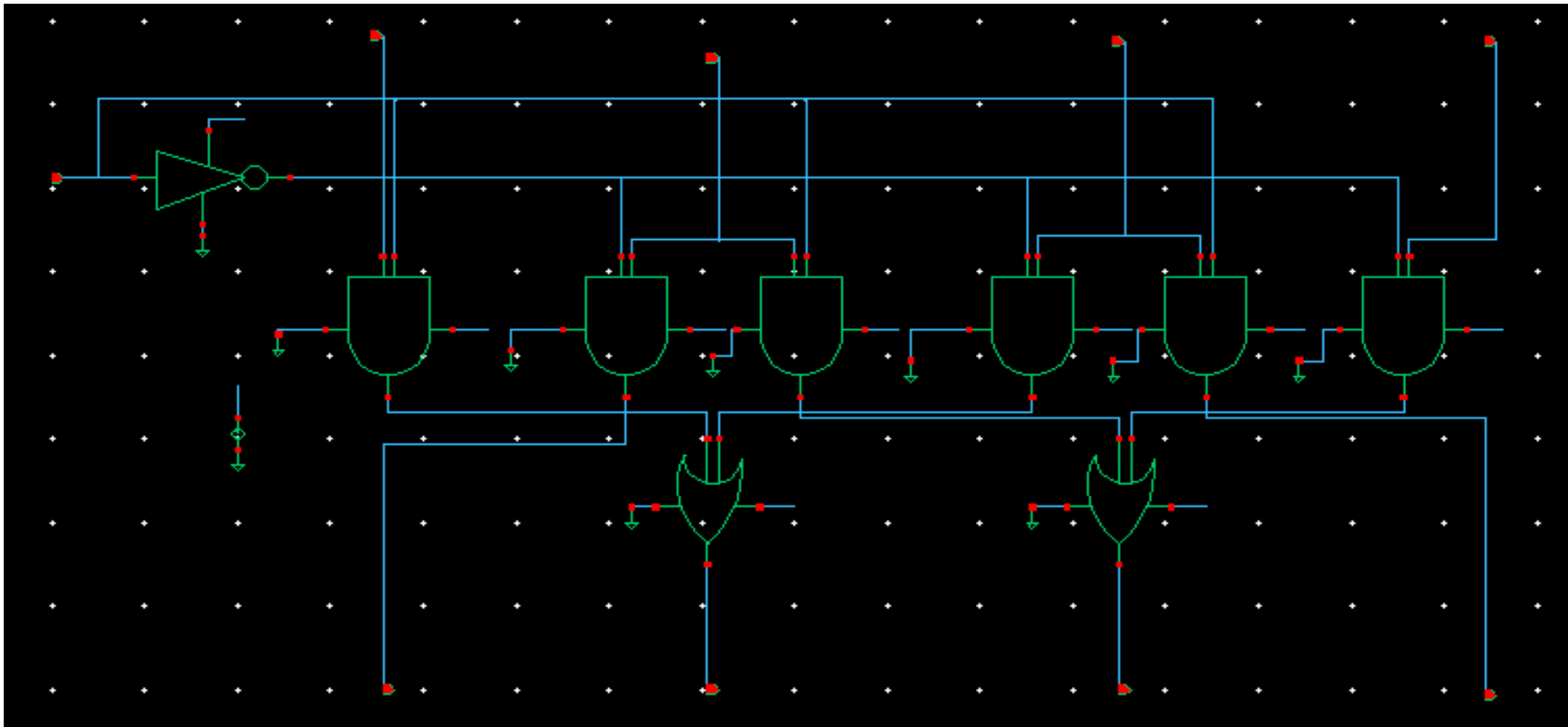 
# 2-bit Binary Shifter Schematic



A **binary left shift** is used to multiply a binary number by two. It consists of shifting all the binary digits to the left by 1 digit and adding an extra digit at the end with a value of 0.




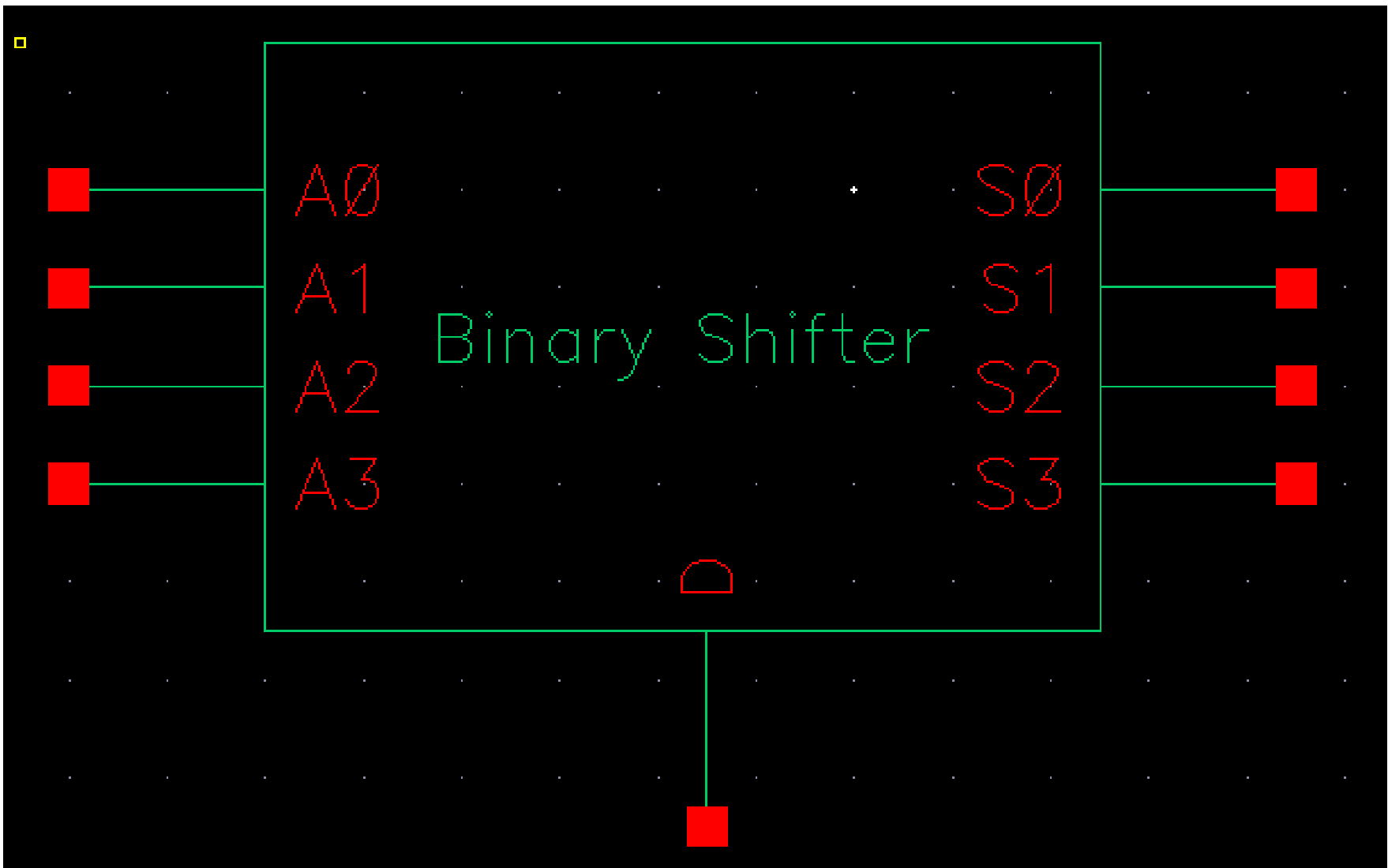
Input D is used to decide whether a **left shift (D=1)** or a **right shift (D=0)** is applied.



# 2-bit Binary Shifter Test

 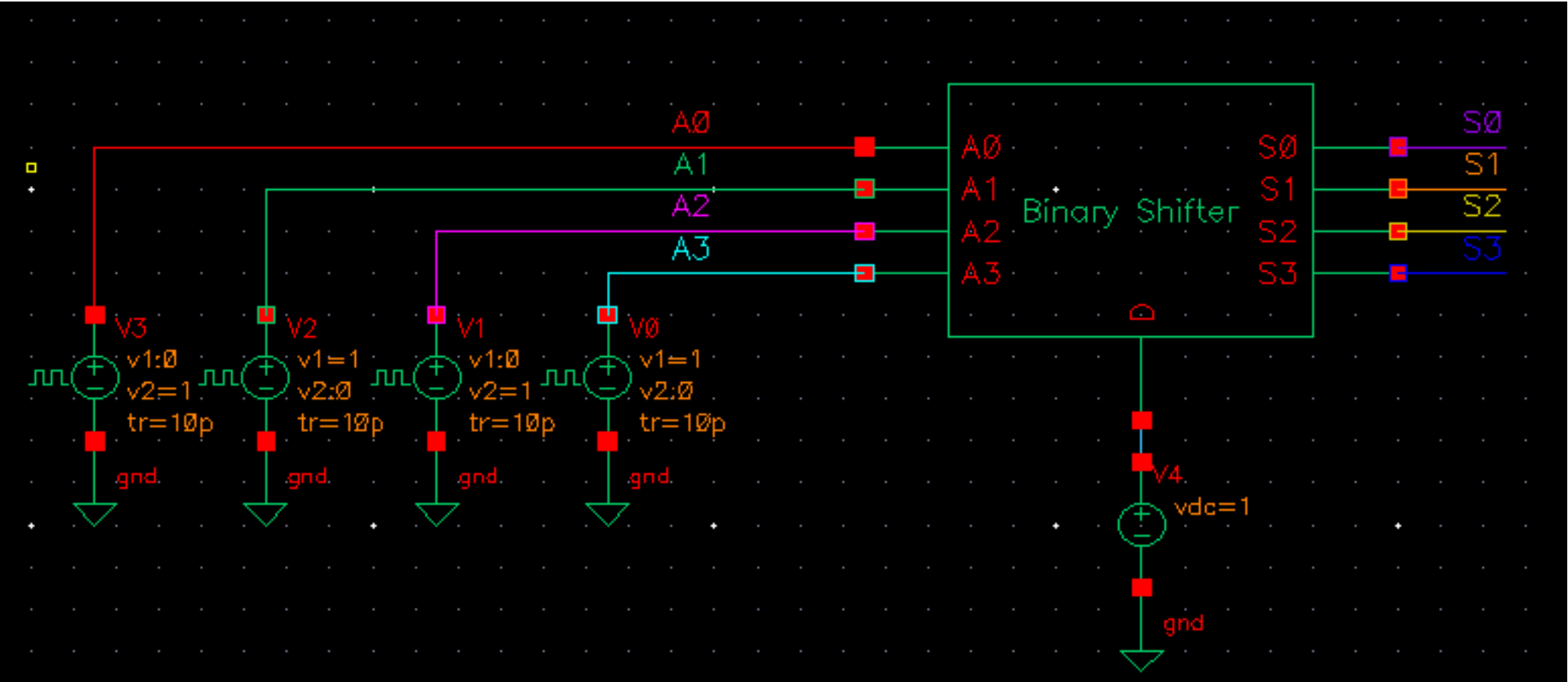


# 4x Binary Shifter

 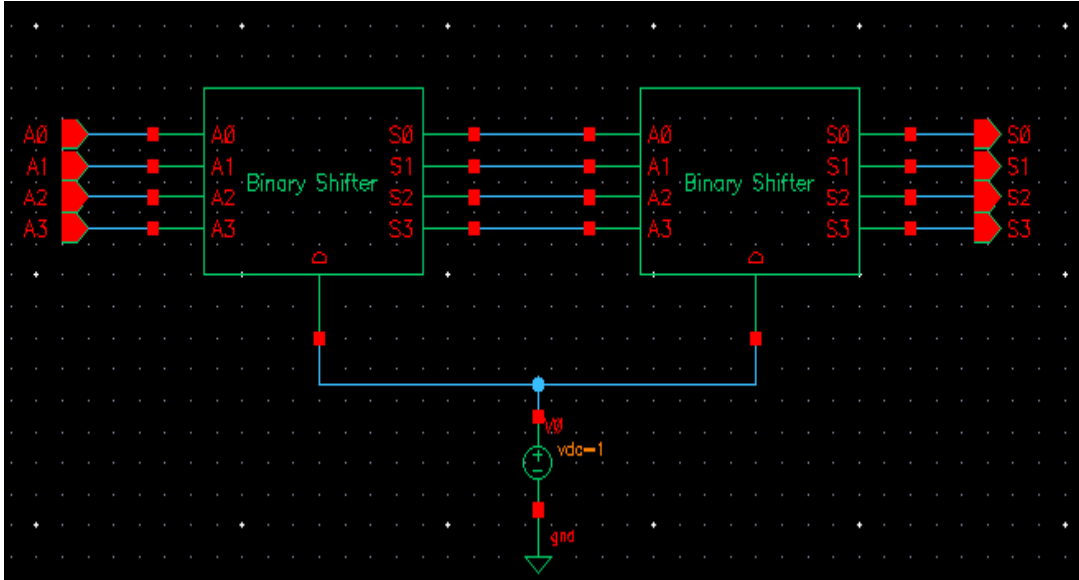

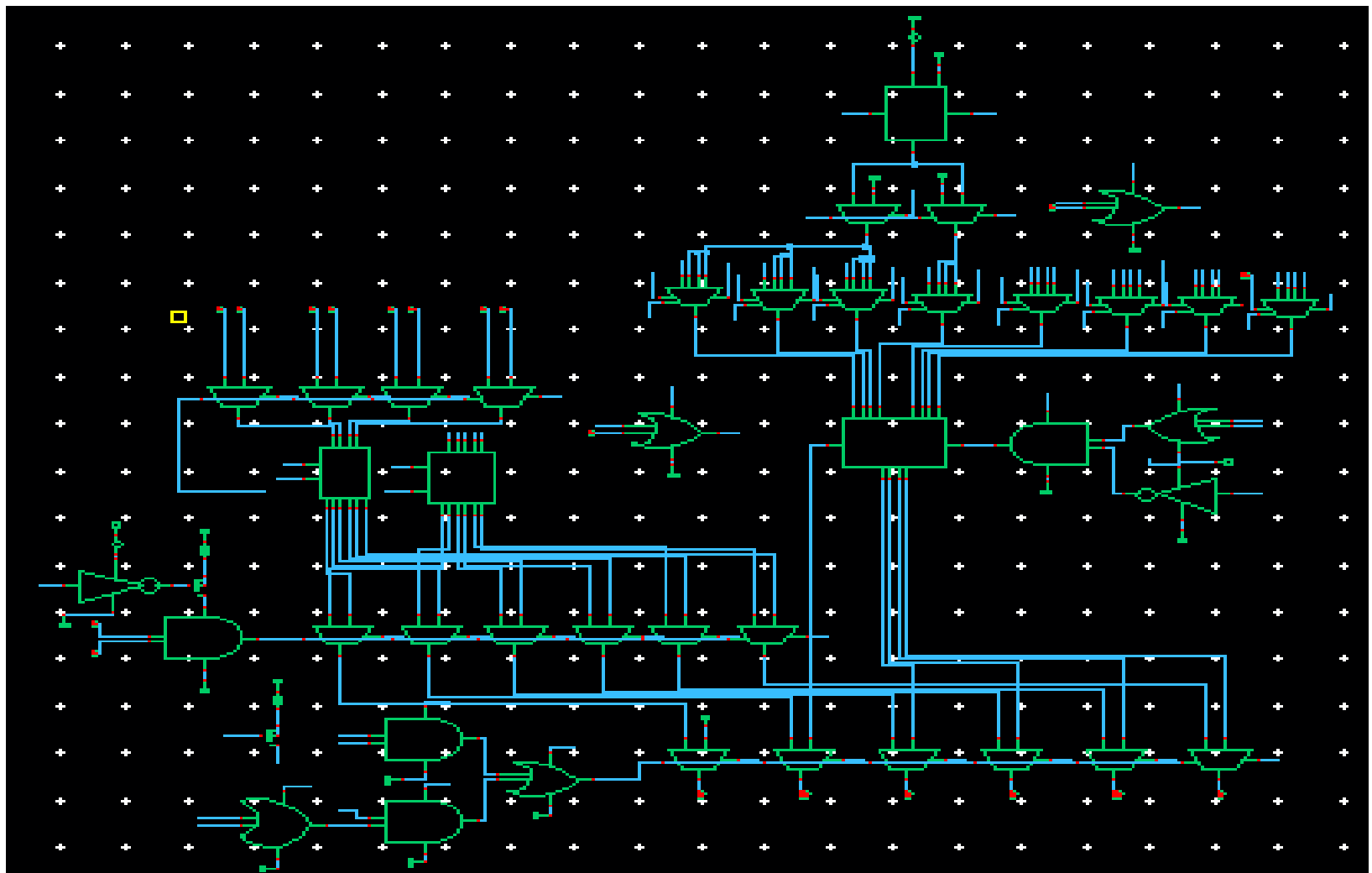
## 4.2 Arithmetic Unit Schematic


- To design the Arithmetic Unit, we incorporate full adders and place two 8x1 multiplexers (MUX) before each full adder. The purpose of these multiplexers is to select the appropriate operation based on our three selectors. It is important to note that the first full adder requires three MUXs, while the subsequent full adders utilize two MUXs each. This selection mechanism allows us to choose the desired operation within the Arithmetic Unit based on the given selectors.




## Arithmetic Unit Symbol

 


# Arithmetic Unit Test

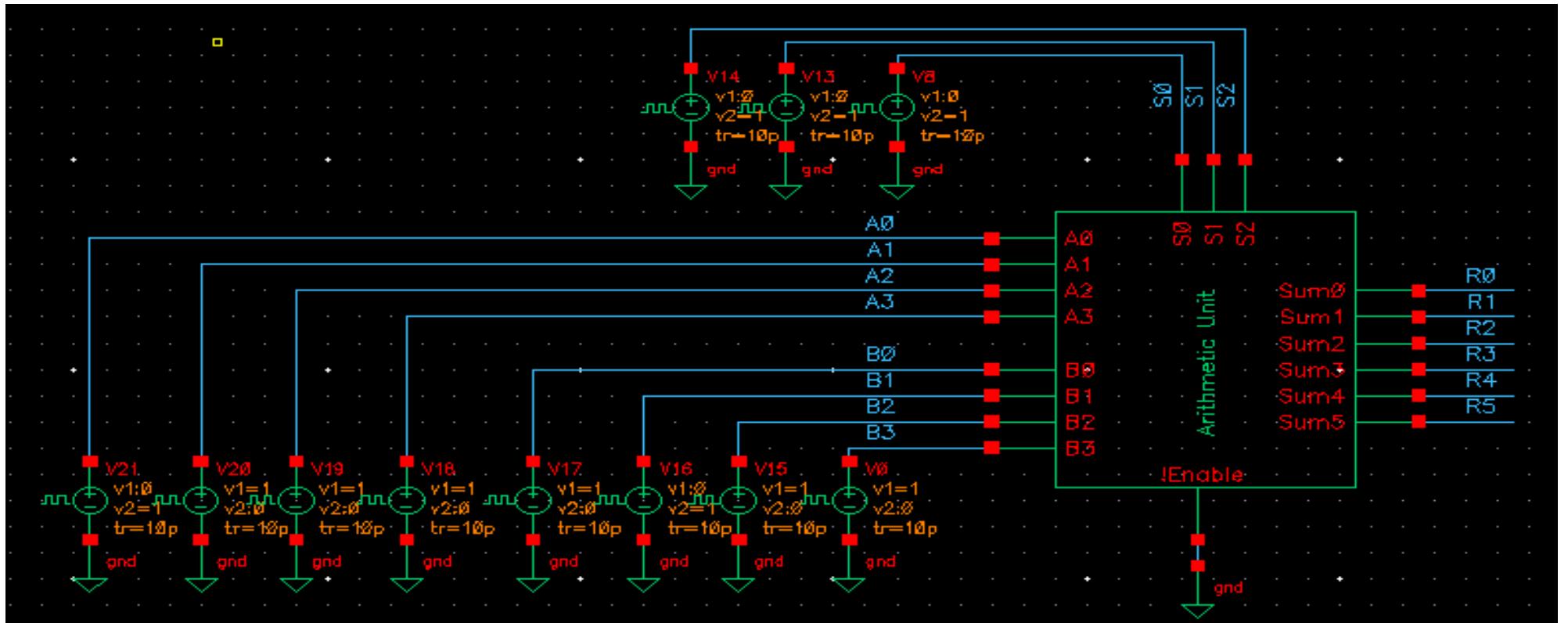

 Testcase:  $Va = 1110, Vb = 1101, S = 000, Result = 001111$




 Testcase:  $Va = 0001, Vb = 0010, S = 001, Result = 010000$






 
Testcase:  $Va = 1110, Vb = 0010, S = 010, Result = 011100$



 
Testcase:  $Va = 0001, Vb = 0010, S = 111, Result = 000100$



 Testcase:  $Va = 1110, Vb = 1101, S = 100, Result = 011100$



 
Testcase:  $Va = 0001, Vb = 0010, S = 101, Result = 000100$



## 5. ALU Design
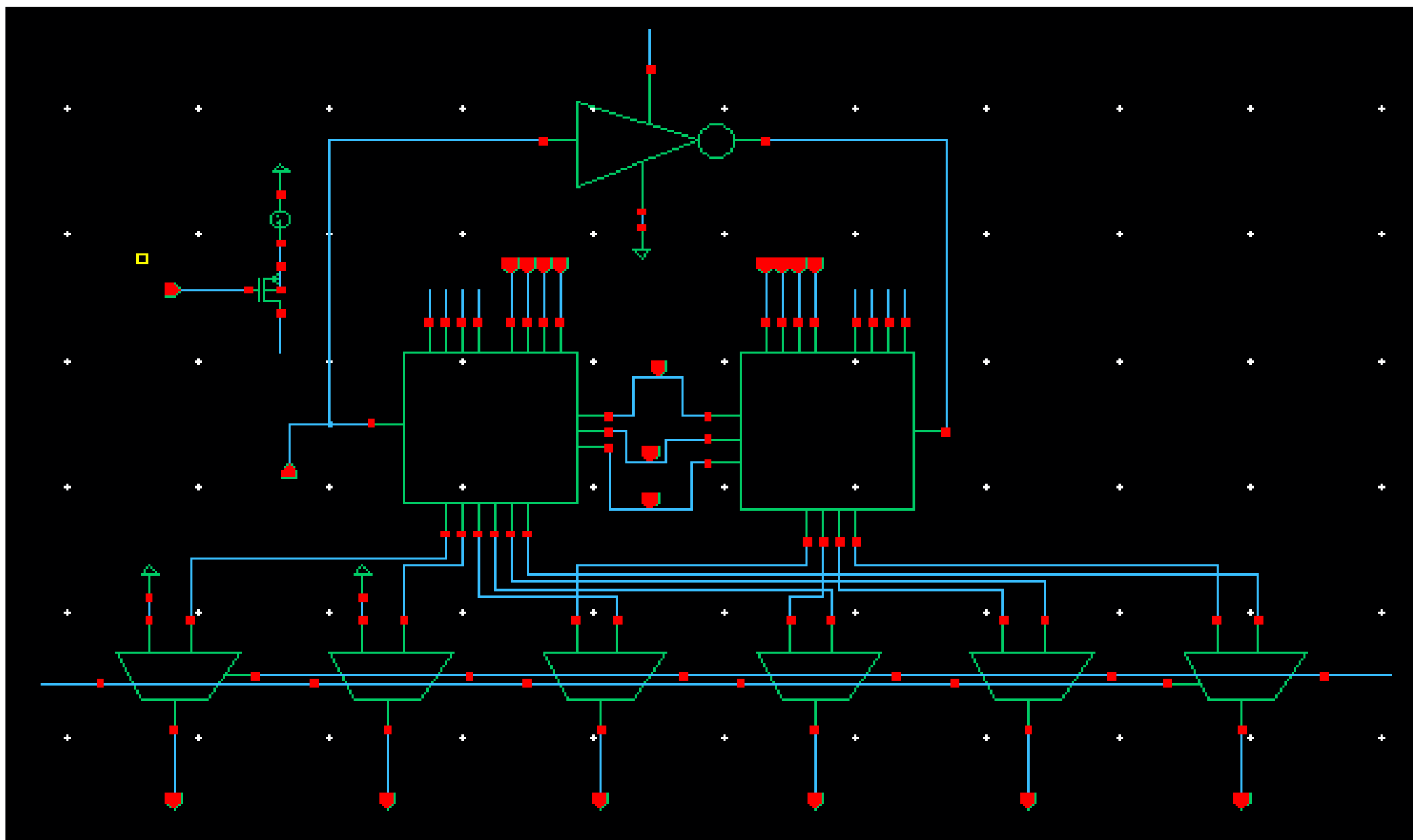
### 5.1 ALU Schematic

- To incorporate both logical and arithmetic operations within the ALU, an additional selector line,  $S3$ , is required.  $S3$  serves as the most significant bit of the selectors and distinguishes between the two types of operations. If  $S3 = 1$ , the operation is a logical one, while if  $S3 = 0$ , it is an arithmetic operation.
- Furthermore, it is important to note that the output of the logic unit consists of 4 bits, whereas the output of the arithmetic unit is 6 bits. To ensure consistency in output length, the last two bits of the logic unit output is set to always be zero (grounded). This adjustment allows for uniformity in the bit length of the ALU's output.



## ALU Symbol

